

Digital Design & Computer Architecture




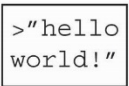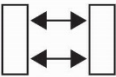
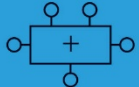

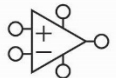

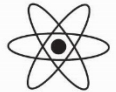
Sarah Harris & David Harris

Chapter 2: Combinational Logic Design

Modified by Younghwan Yoo, 2023

Chapter 2 :: Topics

- **Combinational Circuits**
- **Boolean Equations**
- **Boolean Algebra**
- **From Logic to Gates**
- **X's and Z's, Oh My**
- **Karnaugh Maps**
- **Combinational Building Blocks**
- **Timing**

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	


Chapter 2: Combinational Logic

Combinational Circuits

Introduction

A logic circuit is composed of:

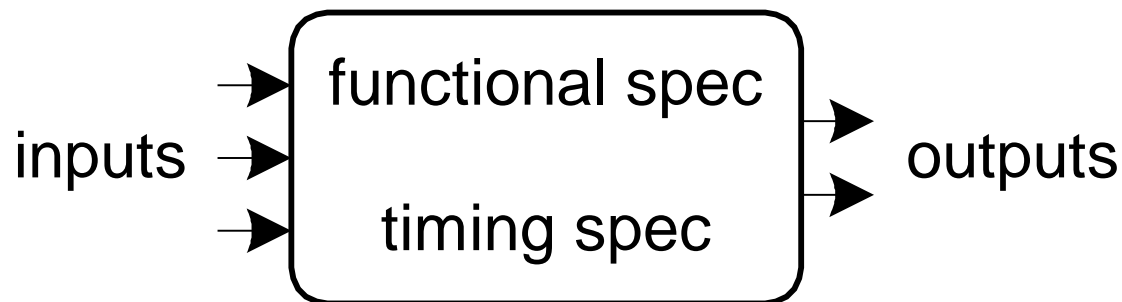- Inputs
- Outputs
- Functional specification
- Timing specification




Circuits

- **Nodes**

- Inputs: A, B, C
- Outputs: Y, Z
- Internal: $n1$

- **Circuit elements**

- $E1, E2, E3$
- Each itself a circuit

 


Types of Logic Circuits

- **Combinational logic**

- Memoryless
- Outputs determined by current values of inputs


- **Sequential logic**

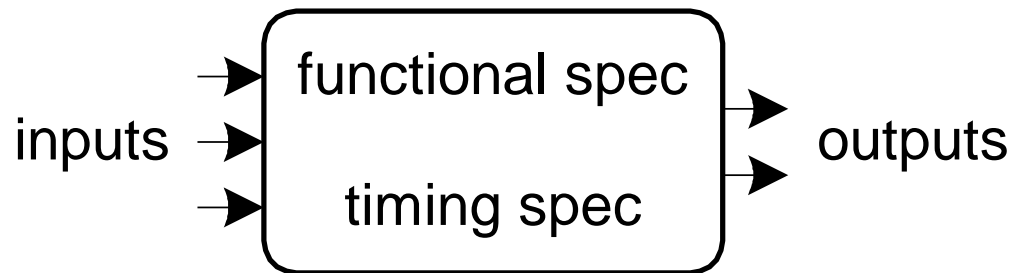- Has memory
- Outputs determined by previous and current values of inputs



Rules of Combinational Composition

- Every element is combinational
- Every node is either an input or connects to *exactly one* output
- The circuit contains no cyclic paths
- **Example:**

 


Chapter 2: Combinational Logic

Boolean Equations

Boolean Equations

- Functional specification of outputs in terms of inputs

 - Example:** $S = F(A, B, C_{in})$
 $C_{out} = F(A, B, C_{in})$



$$S = A \oplus B \oplus C_{in}$$
$$C_{out} = AB + AC_{in} + BC_{in}$$

Some Definitions

- **Complement:** variable with a bar over it
 $\bar{A}, \bar{B}, \bar{C}$
- **Literal:** variable or its complement
 $A, \bar{A}, B, \bar{B}, C, \bar{C}$
- **Implicant:** product of literals
 $AB\bar{C}, \bar{A}C, BC$
- **Minterm:** product that includes all input variables
 $AB\bar{C}, A\bar{B}\bar{C}, ABC$
- **Maxterm:** sum that includes all input variables
 $(A+\bar{B}+C), (\bar{A}+B+\bar{C}), (\bar{A}+\bar{B}+C)$

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where output is **1**
- Thus, a **sum** (OR) of **products** (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) =$$

Sum-of-Products (SOP) Form

- All Boolean equations can be written in SOP form
- Each row has a **minterm**
- A minterm is a **product** (AND) of literals
- Each minterm is **TRUE** for that row (and only that row)
- Form function by **ORing minterms** where output is **1**
- Thus, a **sum** (OR) of **products** (AND terms)

A	B	Y	minterm	minterm name
0	0	0	$\overline{A} \overline{B}$	m_0
0	1	1	$\overline{A} B$	m_1
1	0	0	$A \overline{B}$	m_2
1	1	1	$A B$	m_3

$$Y = F(A, B) = \overline{A}B + AB = \Sigma(m_1, m_3) = \Sigma(\mathbf{1}, \mathbf{3})$$

Long-hand

Short-hand

Product-of-Sums (POS) Form

- All Boolean equations can be written in POS form
- Each row has a **maxterm**
- A maxterm is a **sum** (OR) of literals
- Each maxterm is **FALSE** for that row (and only that row)
- Form function by **ANDing maxterms** where output is **0**
- Thus, a **product** (AND) of **sums** (OR terms)

A	B	Y	maxterm	maxterm name
0	0	0	$A + B$	M_0
0	1	1	$A + \overline{B}$	M_1
1	0	0	$\overline{A} + B$	M_2
1	1	1	$\overline{A} + \overline{B}$	M_3

$$Y = F(A, B) = (A + B) \bullet (\overline{A} + B) = \Pi(\mathbf{0}, \mathbf{2})$$

Long-handShort-hand

Boolean Equations Example

- You are going to the cafeteria for lunch
 - You won't eat lunch ($E = 0$)
 - If it's not clean ($C = 0$) or
 - If they only serve meatloaf ($M = 1$)
- Write a truth table for determining if you will eat lunch (E).

C	M	E
0	0	
0	1	
1	0	
1	1	

SOP & POS Form

SOP – sum-of-products

C	M	E	minterm
0	0	0	$\overline{C} \overline{M}$
0	1	0	$\overline{C} M$
1	0	1	$C \overline{M}$
1	1	0	$C M$

POS – product-of-sums

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \overline{M}$
1	0	1	$\overline{C} + M$
1	1	0	$\overline{C} + \overline{M}$

SOP & POS Form

SOP – sum-of-products

C	M	E	minterm
0	0	0	$\overline{C} \overline{M}$
0	1	0	$\overline{C} M$
1	0	1	$C \overline{M}$
1	1	0	$C M$

$$\begin{aligned} E &= C\overline{M} \\ &= \Sigma(2) \end{aligned}$$

POS – product-of-sums

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \overline{M}$
1	0	1	$\overline{C} + M$
1	1	0	$\overline{C} + \overline{M}$

$$\begin{aligned} E &= (C + M)(C + \overline{M})(\overline{C} + \overline{M}) \\ &= \Pi(0, 1, 3) \end{aligned}$$

Forming Boolean Expressions

Example 1:

We will go to the Park (***P*** is the output) if it's not Raining (\overline{R}) and we have Sandwiches (***S***).

Boolean Equation:

Forming Boolean Expressions

Example 2:

You will be considered a Winner (**W** is the output) if we send you a Million dollars (**M**) or a small Notepad (**N**).

Boolean Equation:

Forming Boolean Expressions

Example 3:

You can Eat delicious food (E is the output) if you Make it yourself (M) or you have a personal Chef (C) and she/he is talented (T) but not eXpensive (\bar{X}).

Boolean Equation:

Forming Boolean Expressions

Example 4:

You can Enter the building if you have a Hat and Shoes on or if you have a Hat on.

Boolean Equation:

Forming Boolean Expressions

Example 5:

You can Enter the building if you have a Hat and Shoes on or if you have a Hat and no Shoes on.

Boolean Equation:

Chapter 2: Combinational Logic

Boolean Algebra: Axioms

Boolean Algebra

- Axioms and theorems to **simplify** Boolean equations
- Like regular algebra, but simpler: variables have only two values (1 or 0)
- **Duality** in axioms and theorems:
 - ANDs and ORs, 0's and 1's interchanged

Boolean Axioms

Number	Axiom	Name
A1	$B = 0 \text{ if } B \neq 1$	Binary Field
A2	$\bar{0} = 1$	NOT
A3	$0 \bullet 0 = 0$	AND/OR
A4	$1 \bullet 1 = 1$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	AND/OR

Boolean Axioms

Number	Axiom	Dual	Name
A1	$B = 0 \text{ if } B \neq 1$	$B = 1 \text{ if } B \neq 0$	Binary Field
A2	$\overline{0} = 1$	$\overline{1} = 0$	NOT
A3	$0 \bullet 0 = 0$	$1 + 1 = 1$	AND/OR
A4	$1 \bullet 1 = 1$	$0 + 0 = 0$	AND/OR
A5	$0 \bullet 1 = 1 \bullet 0 = 0$	$1 + 0 = 0 + 1 = 1$	AND/OR

Dual: Replace: \bullet with $+$
 0 with 1
 1 with 0

Chapter 2: Combinational Logic

Boolean Algebra: Theorems of One Variable

Boolean Theorems of One Variable

Number	Theorem	Name
T1	$B \bullet 1 = B$	Identity
T2	$B \bullet 0 = 0$	Null Element
T3	$B \bullet B = B$	Idempotency
T4	$\overline{\overline{B}} = B$	Involution
T5	$B \bullet \overline{B} = 0$	Complements

Dual: Replace: \bullet with $+$
 0 with 1
 1 with 0



Boolean Theorems of One Variable

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	$B + \overline{B} = 1$	Complements

Dual: Replace: \bullet with $+$
0 with 1
1 with 0


T1: Identity Theorem

- $B \cdot 1 = B$
- $B + 0 = B$

  



T2: Null Element Theorem

- $B \cdot 0 = 0$
- $B + 1 = 1$

 


T3: Idempotency Theorem

- $B \cdot B = B$
- $B + B = B$

  



T4: Identity Theorem

- $\overline{\overline{B}} = B$

 

T5: Complement Theorem

  - $B \cdot \bar{B} = 0$
- $B + \bar{B} = 1$



Recap: Basic Boolean Theorems

Number	Theorem	Dual	Name
T1	$B \bullet 1 = B$	$B + 0 = B$	Identity
T2	$B \bullet 0 = 0$	$B + 1 = 1$	Null Element
T3	$B \bullet B = B$	$B + B = B$	Idempotency
T4	$\overline{\overline{B}} = B$		Involution
T5	$B \bullet \overline{B} = 0$	$B + \overline{B} = 1$	Complements

Chapter 2: Combinational Logic

Boolean Algebra: Theorems of Several Variables

Boolean Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \bar{C}) = B$	$(B + C) \bullet (B + \bar{C}) = B$	Combining
T11	$(B \bullet C) + (\bar{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\bar{B} \bullet D)$	$(B + C) \bullet (\bar{B} + D) \bullet (C + D) = (B + C) \bullet (\bar{B} + D)$	Consensus

Warning: T8' differs from traditional algebra:
OR (+) distributes over AND (\bullet)

How to Prove

- **Method 1:** Perfect induction
- **Method 2:** Use other theorems and axioms to simplify the equation
 - Make one side of the equation look like the other

Proof by Perfect Induction

- Also called: **proof by exhaustion**
- Check every possible input value
- If the two expressions produce the same value for every possible input combination, the expressions are equal

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Prove true by:

- **Method 1:** Perfect induction
- **Method 2:** Using other theorems and axioms

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 1: Perfect Induction

B	C	$(B+C)$	$B(B+C)$
0	0	0	0
0	1	1	0
1	0	1	1
1	1	1	1

T9: Covering

Number	Theorem	Name
T9	$B \bullet (B+C) = B$	Covering

Method 2: Prove true using other axioms and theorems.

$$\begin{aligned} B \bullet (B+C) &= B \bullet B + B \bullet C \\ &= \mathbf{B} + B \bullet C \\ &= \mathbf{B \bullet 1} + B \bullet C \\ &= B \bullet (1 + C) \\ &= B \bullet (\mathbf{1}) \\ &= B \end{aligned}$$

T8: Distributivity

T3: Idempotency

T1: Identity

T8: Distributivity

T2: Null element

T1: Identity

T10: Combining

Number	Theorem	Name
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	Combining

Prove true using other axioms and theorems:

$$\begin{aligned} B \bullet C + B \bullet \overline{C} &= B \bullet (C + \overline{C}) && \text{T8: Distributivity} \\ &= B \bullet (1) && \text{T5': Complements} \\ &= B && \text{T1: Identity} \end{aligned}$$

De Morgan's Theorem: Dual

#	Theorem	Dual	Name
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B + C + D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's Theorem

The **complement** of the **product** is the **sum** of the **complements**.

Dual:

The **complement** of the **sum** is the **product** of the **complements**.

Recap: Theorems of Several Vars

#	Theorem	Dual	Name
T6	$B \bullet C = C \bullet B$	$B + C = C + B$	Commutativity
T7	$(B \bullet C) \bullet D = B \bullet (C \bullet D)$	$(B + C) + D = B + (C + D)$	Associativity
T8	$B \bullet (C + D) = (B \bullet C) + (B \bullet D)$	$B + (C \bullet D) = (B + C) (B + D)$	Distributivity
T9	$B \bullet (B + C) = B$	$B + (B \bullet C) = B$	Covering
T10	$(B \bullet C) + (B \bullet \overline{C}) = B$	$(B + C) \bullet (B + \overline{C}) = B$	Combining
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) = (B \bullet C) + (\overline{B} \bullet D)$	$(B + C) \bullet (\overline{B} + D) \bullet (C + D) = (B + C) \bullet (\overline{B} + D)$	Consensus
T12	$\overline{B \bullet C \bullet D \dots} = \overline{B} + \overline{C} + \overline{D} \dots$	$\overline{B + C + D \dots} = \overline{B} \bullet \overline{C} \bullet \overline{D} \dots$	De Morgan's

Chapter 2: Combinational Logic

Boolean Algebra: Simplifying Equations

Simplifying an Equation

Simplifying may mean minimal sum of products form:

- SOP form that has the **fewest number of implicants**, where each implicant has the **fewest literals**
 - **Implicant:** product of literals
 $\overline{A}\overline{B}C, A\overline{C}, B\overline{C}$
 - **Literal:** variable or its complement
 $A, \overline{A}, B, \overline{B}, C, \overline{C}$

Simplifying could also mean fewest number of gates, lowest cost, lowest power, etc. For example, $Y = A \text{ XOR } B$ is likely simpler than minimal Sum of Products $Y = A\overline{B} + \overline{A}B$. These depend on details of the technology.


Simplifying Boolean Equations

Example 1:

$$Y = \bar{A}B + AB$$

$$Y = B$$

T10: Combining

 

or

$$Y = B(A + \bar{A})$$

T8: Distributivity

$$= B(1)$$

T5': Complements

$$= B$$

T1: Identity

Simplifying Boolean Equations

Example 2:

$$Y = \bar{A}\bar{B}C + ABC + \bar{A}BC$$

$$= \bar{A}\bar{B}C + \textcolor{red}{ABC} + \textcolor{red}{ABC} + \bar{A}BC \quad \text{T3': Idempotency}$$

$$= (\textcolor{red}{\bar{A}\bar{B}C + ABC}) + (\textcolor{blue}{ABC + \bar{A}BC}) \quad \text{T7': Associativity}$$

$$= \textcolor{red}{AC} + \textcolor{blue}{BC} \quad \text{T10: Combining}$$

Chapter 2: Combinational Logic

Extra Examples

Boolean Algebra: Simplifying Equations

Simplification Methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{P}A + PA = P$
- **Expansion**
 $P = \overline{P}A + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Proving the “Simplification” Theorem

“Simplification” theorem

$$A + \bar{A}P = A + P$$

Method 1: $A + \bar{A}P = A + AP + \bar{A}P$
 $= A + (AP + \bar{A}P)$
 $= A + P$

T9' Covering

T7 Associativity

T10 Combining

Method 2: $A + \bar{A}P = (A + \bar{A})(A + P)$
 $= 1 \cdot (A + P)$
 $= A + P$

T8' Distributivity

T5' Complements

T1 Identity

T11: Consensus

Number	Theorem	Name
T11	$(B \bullet C) + (\overline{B} \bullet D) + (C \bullet D) =$ $(B \bullet C) + (\overline{B} \bullet D)$	Consensus

Prove using other theorems and axioms:

$$\begin{aligned}
 & \mathbf{B \bullet C + \overline{B} \bullet D + C \bullet D} \\
 &= BC + \overline{B}D + (CDB + C\overline{D}B) \\
 &= BC + \overline{B}D + \mathbf{BCD} + \overline{B}CD \\
 &= \mathbf{BC} + \mathbf{BCD} + \overline{B}D + \overline{B}CD \\
 &= \mathbf{BC}(1 + D) + \overline{B}D(1 + C) \\
 &= \mathbf{BC} + \overline{B}D
 \end{aligned}$$

T10: Combining

T6: Commutativity

T6: Commutativity

T8: Distributivity

T2': Null Element

Simplification Methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{P}A + PA = P$
- **Expansion**
 $P = \overline{P}A + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplification Methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{PA} + PA = P$
- **Expansion**
 $P = \overline{PA} + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplifying Boolean Equations

Example 3:

$$Y = A(AB + ABC)$$

$$= A(AB(1 + C))$$

$$= A(AB(1))$$

$$= A(AB)$$

$$= (AA)B$$

$$= AB$$

T8: Distributivity

T2': Null Element

T1: Identity

T7: Associativity

T3: Idempotency

Simplification Methods

- **Distributivity (T8, T8')**
 $B(C+D) = BC + BD$
 $B + CD = (B+C)(B+D)$
- **Covering (T9')**
 $A + AP = A$
- **Combining (T10)**
 $\overline{P}A + PA = P$
- **Expansion**
 $P = \overline{P}A + PA$
 $A = A + AP$
- **Idempotency (duplication)** $A = A + A$
- **“Simplification” theorem**
 $A + \overline{A}P = A + P$
 $\overline{A} + AP = \overline{A} + P$

Simplifying Boolean Equations

Example 4:

$$Y = A'BC + A'$$

$$= A'$$

or

$$= A'(BC + 1)$$

$$= A'(1)$$

$$= A'$$

$$\text{Recall: } A' = \bar{A}$$

$$\text{T9' Covering: } X + XY = X$$

T8: Distributivity

T2': Null Element

T1: Identity

Multiplying Out: SOP Form

An expression is in **sum-of-products (SOP)** form when all products contain literals only.

- **SOP form:** $Y = AB + BC' + DE$
- **NOT SOP form:** $Y = DF + E(A' + B)$
- **SOP form:** $Z = A + BC + DE'F$

Multiplying Out: SOP Form

Example 5:

$$Y = (A + C + D + E)(A + B)$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $X = (C+D+E)$, $Z = B$ and rewrite equation

$Y = (A + \textcolor{red}{X})(A + \textcolor{blue}{Z})$	substitution ($\textcolor{red}{X} = (C+D+E)$, $\textcolor{blue}{Z} = B$)
$= A + \textcolor{red}{X}\textcolor{blue}{Z}$	T8': Distributivity
$= A + (\textcolor{red}{C+D+E})\textcolor{blue}{B}$	substitution
$= A + BC + BD + BE$	T8: Distributivity

or

$Y = AA + AB + AC + BC + AD + BD + AE + BE$	T8: Distributivity
$= \textcolor{red}{A} + AB + AC + AD + AE + BC + BD + BE$	T3: Idempotency
$= \textcolor{red}{A} + \quad \quad \quad BC + BD + BE$	T9': Covering

This method is called ***multiplying out.***

Simplifying Boolean Equations

Example 6:

$$Y = AB + BC + B'D' + AC'D'$$

Method 1:

$$\begin{aligned} Y &= AB + BC + B'D' + (ABC'D' + AB'C'D') && \text{T10: Combining} \\ &= (AB + ABC'D') + BC + (B'D' + AB'C'D') && \text{T6: Commutat.} \\ & && \text{T7: Associativity} \\ &= AB + BC + B'D' && \text{T9: Covering} \end{aligned}$$

Method 2:

$$\begin{aligned} Y &= AB + BC + B'D' + AC'D' + AD' && \text{T11: Consensus} \\ &= AB + BC + B'D' + AD' && \text{T9: Covering} \\ &= AB + BC + B'D' && \text{T11: Consensus} \end{aligned}$$

Literal and implicant ordering

- Variables within an implicant should be in alphabetical order.
- The order of implicants doesn't matter.

Examples:

- **Correct:** $Y = AB + BC + \bar{B}\bar{D}$
- **Correct:** $Y = BC + \bar{B}\bar{D} + AB$
- **Incorrect:** $Y = \textcolor{red}{CB} + \bar{B}\bar{D} + \textcolor{red}{BA}$
- **Incorrect:** $Y = AB + BC + \textcolor{red}{\bar{D}\bar{B}}$

Simplifying Boolean Equations

Example 7:

$$Y = (A + BC)(A + DE)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = BC$, $Z = DE$ and rewrite equation

$$\begin{aligned} Y &= (A + \textcolor{red}{X})(A + \textcolor{blue}{Z}) && \text{substitution } (\textcolor{red}{X}=BC, \textcolor{blue}{Z}=DE) \\ &= A + \textcolor{red}{X}\textcolor{blue}{Z} && \text{T8': Distributivity} \\ &= A + \textcolor{red}{BC}\textcolor{blue}{DE} && \text{substitution} \end{aligned}$$

or

$$\begin{aligned} Y &= AA + ADE + ABC + BCDE && \text{T8: Distributivity} \\ &= A + ADE + ABC + BCDE && \text{T3: Idempotency} \\ &= \textcolor{black}{A} + \textcolor{black}{ADE} + \textcolor{black}{ABC} + BCDE \\ &= \textcolor{black}{A} + BCDE && \text{T9': Covering} \\ &= A + BCDE && \text{T9': Covering} \end{aligned}$$

Review: Canonical SOP & POS Forms

SOP – sum-of-products $E = \boxed{C\bar{M}}$

C	M	E	minterm
0	0	0	$\bar{C} \bar{M}$
0	1	0	$\bar{C} M$
1	0	1	$C \bar{M}$
1	1	0	$C M$

same

POS – product-of-sums $E = (C + M)(C + \bar{M})(\bar{C} + \bar{M})$

C	M	E	maxterm
0	0	0	$C + M$
0	1	0	$C + \bar{M}$
1	0	1	$\bar{C} + M$
1	1	0	$\bar{C} + \bar{M}$

$$\begin{aligned}
 &= (C + M\bar{M})^* (\bar{C} + \bar{M}) \\
 &= (C + 0)^* (\bar{C} + \bar{M}) \\
 &= C^* (\bar{C} + \bar{M}) \\
 &= C\bar{C} + C\bar{M} \\
 &= 0 + C\bar{M} \\
 &= \boxed{C\bar{M}}
 \end{aligned}$$

Factoring: POS Form

An expression is in **product-of-sums (POS)** form when all sums contain literals only.

- **POS form:** $Y = (A+B)(C+D)(E'+F)$
- **NOT POS form:** $Y = (D+E)(F'+GH)$
- **POS form:** $Z = A(B+C)(D+E')$

Factoring: POS Form

Example 8:

$$Y = (A + B' C D E)$$

Apply T8' first when possible: $W + XZ = (W + X)(W + Z)$

Make: $X = B'C$, $Z = DE$ and rewrite equation

$Y = (A + XZ)$	substitution ($X = B'C$, $Z = DE$)
$= (A + B'C)(A + DE)$	T8': Distributivity
$= (A + B')(A + C)(A + D)(A + E)$	T8': Distributivity

Factoring: POS Form

Example 9:

$$Y = AB + C'DE + F$$

Apply T8' first when possible: $W+XZ = (W+X)(W+Z)$

Make: $W = AB$, $X = C'$, $Z = DE$ and rewrite equation

$Y = (W+XZ) + F$	substitution $W = AB$, $X = C'$, $Z = DE$
$= (W+X)(W+Z) + F$	T8': Distributivity
$= (AB+C')(AB+DE)+F$	substitution
$= (A+C')(B+C')(AB+D)(AB+E)+F$	T8': Distributivity
$= (A+C')(B+C')(A+D)(B+D)(A+E)(B+E)+F$	T8': Distributivity
$= (A+C'+F)(B+C'+F)(A+D+F)(B+D+F)(A+E+F)(B+E+F)$	T8': Distr.

De Morgan's Theorem

Example 10:

$$\begin{aligned} Y &= \overline{(A+BD)C} \\ &= \overline{(A+\overline{\overline{BD}})} + \overline{\overline{C}} \\ &= (\overline{A} \bullet \overline{\overline{BD}}) + C \\ &= (\overline{A} \bullet (BD)) + C \\ &= \overline{A}BD + C \end{aligned}$$

- Work from the **outside in** (i.e., top bar, then down)
- Use **involution** when possible

De Morgan's Theorem

Example 11:

$$\begin{aligned} Y &= \overline{(\overline{ACE} + \overline{D})} + B \\ &= (\overline{\overline{ACE} + \overline{D}}) \cdot \overline{B} \\ &= (\overline{\overline{ACE}} \cdot \overline{\overline{D}}) \cdot \overline{B} \\ &= ((\overline{\overline{AC}} + \overline{E}) \cdot D) \cdot \overline{B} \\ &= ((AC + \overline{E}) \cdot D) \cdot \overline{B} \\ &= (ACD + D\overline{E}) \cdot \overline{B} \\ &= \overline{A}\overline{B}CD + \overline{B}D\overline{E} \end{aligned}$$

Common Errors

- **Losing bars** (alignment will help you avoid this)
- **Losing terms** (alignment will help you avoid this)
- **Trying to do multiple steps at once** – this is prone to errors!
- **Applying theorems incorrectly**, for example:
 - **Wrong:** $ABC + \overline{A}BC = B$ **Correct:** $ABC + \overline{A}BC = AC$. Products may only **differ in a single term** when using the combining theorem.
 - **Wrong:** $(A + \overline{A}) = 0$ **Correct:** $A + \overline{A} = 1$
 - **Wrong:** $(A \cdot \overline{A}) = 1$ **Correct:** $A \cdot \overline{A} = 0$
 - **Wrong:** $ABC = B$ **Correct:** $B + ABC = B$. In order to use the covering theorem, you must have a term that covers the other terms.
 - **Wrong:** $\overline{AC} = \overline{A}\overline{C}$ **Correct:** $\overline{AC} = \overline{A} + \overline{C}$ (De Morgan's)
 - **Wrong:** $\overline{A + C} = \overline{A} + \overline{C}$ **Correct:** $\overline{A + C} = \overline{A}\overline{C}$ (De Morgan's)


Chapter 2: Combinational Logic

From Logic to Gates

From Logic to Gates


Build the following equation using logic gates:

$$Y = A\bar{B} + \bar{C}DE$$

 

Circuit Schematics Rules

 - Inputs on the left (or top)
- Outputs on right (or bottom)
- Gates flow from left to right
- Straight wires are best




Circuit Schematic Rules (cont.)

- Wires always connect at a T junction
- A dot where wires cross indicates a connection between the wires
- Wires crossing *without* a dot make no connection


wires connect
at a T junction



wires connect
at a dot

 


 wires crossing
without a dot do
not connect



Two-Level Logic


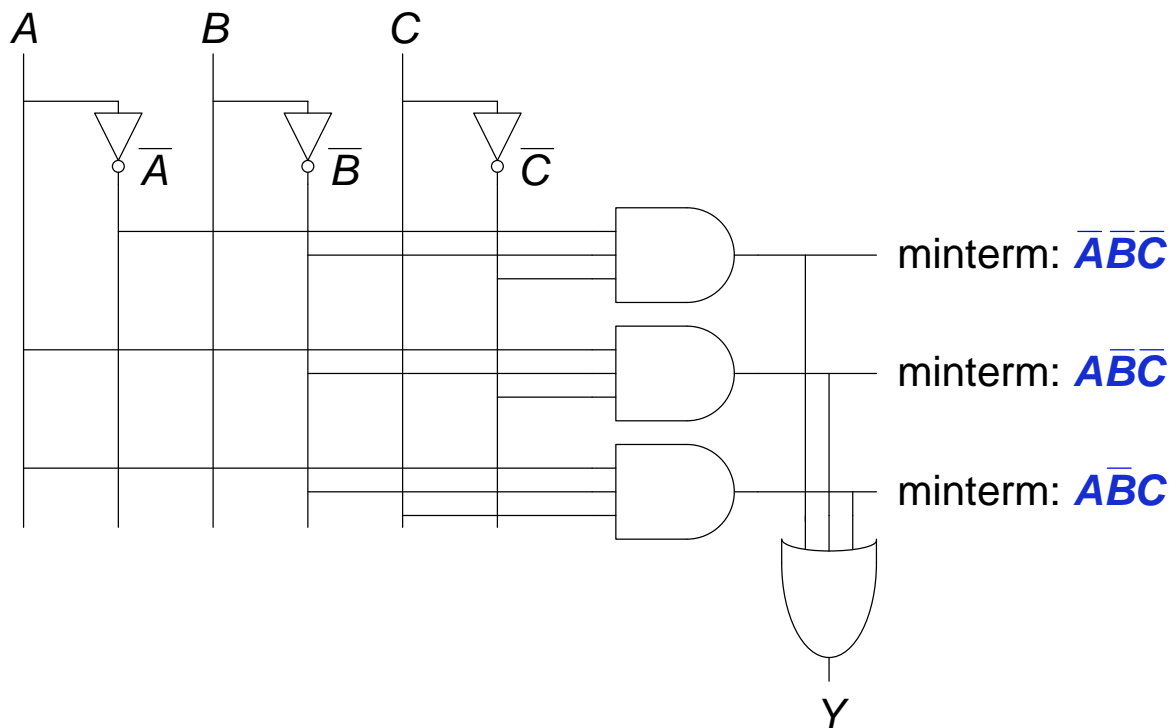
- Two-level logic: **ANDs** followed by **ORs**
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$



Implements functions in **SOP form**

Multilevel Logic

  
- Complex logic is often built from many stages of simpler gates.



Multiple-Output Circuits

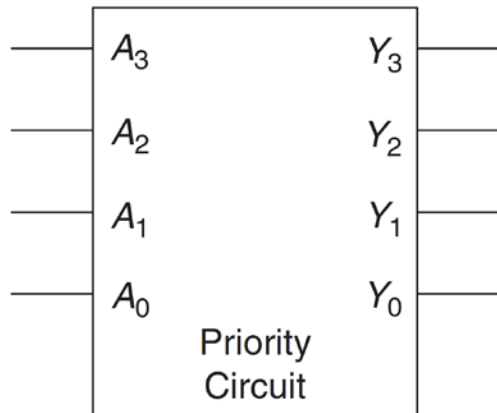- Example: Priority Circuit**

Output asserted
corresponding to most
significant TRUE input



A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

Priority Circuit Hardware


A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

$$Y_3 = A_3$$

$$Y_2 = \overline{A_3} A_2$$

$$Y_1 = \overline{A_3} \overline{A_2} A_1$$
 
$$Y_0 = \overline{A_3} \overline{A_2} \overline{A_1} A_0$$



Don't Cares

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	0
0	1	0	0	0	1	0	0
0	1	0	1	0	1	0	0
0	1	1	0	0	1	0	0
0	1	1	1	0	1	0	0
1	0	0	0	1	0	0	0
1	0	0	1	1	0	0	0
1	0	1	0	1	0	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	0
1	1	0	1	1	0	0	0
1	1	1	0	1	0	0	0
1	1	1	1	1	0	0	0

$$Y_3 = A_3$$

$$Y_2 = \overline{A_3} A_2$$

$$Y_1 = \overline{A_3} \overline{A_2} A_1$$

$$Y_0 = \overline{A_3} \overline{A_2} \overline{A_1} A_0$$

A_3	A_2	A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	X	0	0	1	0
0	1	X	X	0	1	0	0
1	X	X	X	1	0	0	0

Chapter 2: Combinational Logic

Two-Level Logic Forms


Two-Level Logic Variations

- **ANDs** followed by **ORs**: **SOP** form
- **ORs** followed by **ANDs**: **POS** form
- Only **NAND** gates: **SOP** form
- Only **NOR** gates: **POS** form

Most common form of two-level logic

Two-Level Logic Variation

 
- Two-level logic variation: **ORs** followed by **ANDs**
- Example: $Y = (\bar{A} + \bar{B})(A + B + \bar{C})$



Implements functions in **POS form**

Two-Level Logic

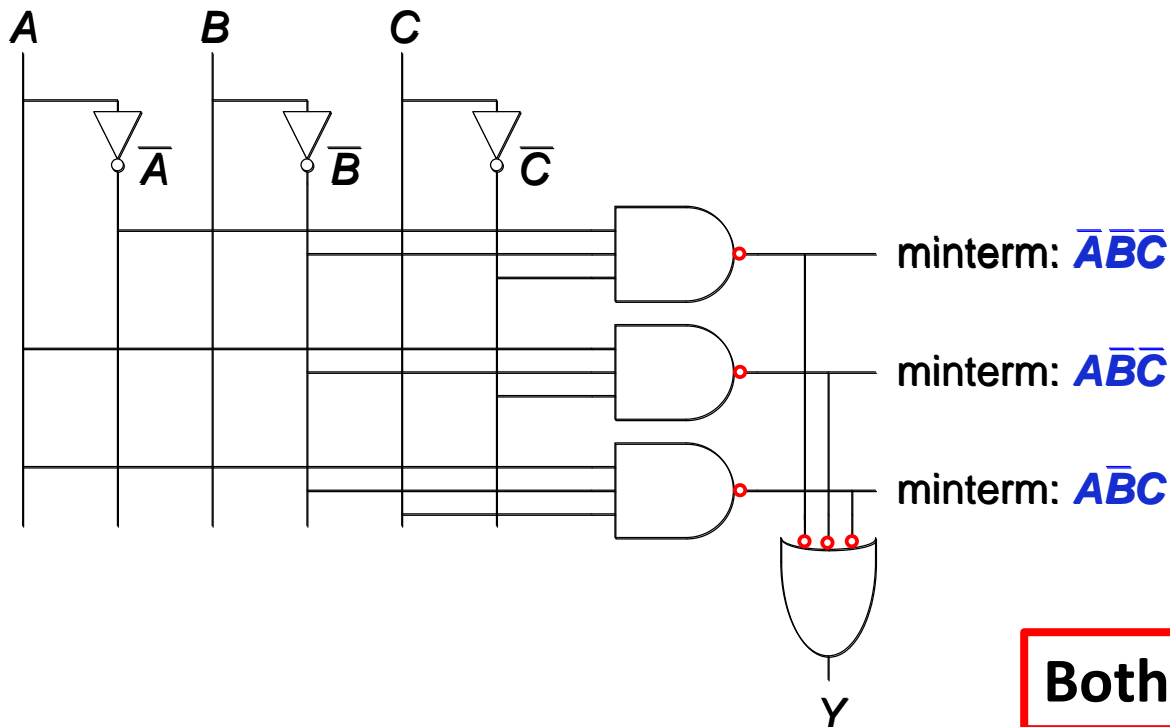
- Two-level logic: **ANDs** followed by **ORs** → **NANDs**
- Example: $Y = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + A\bar{B}C$



Both: SOP form

Two-Level Logic Variation

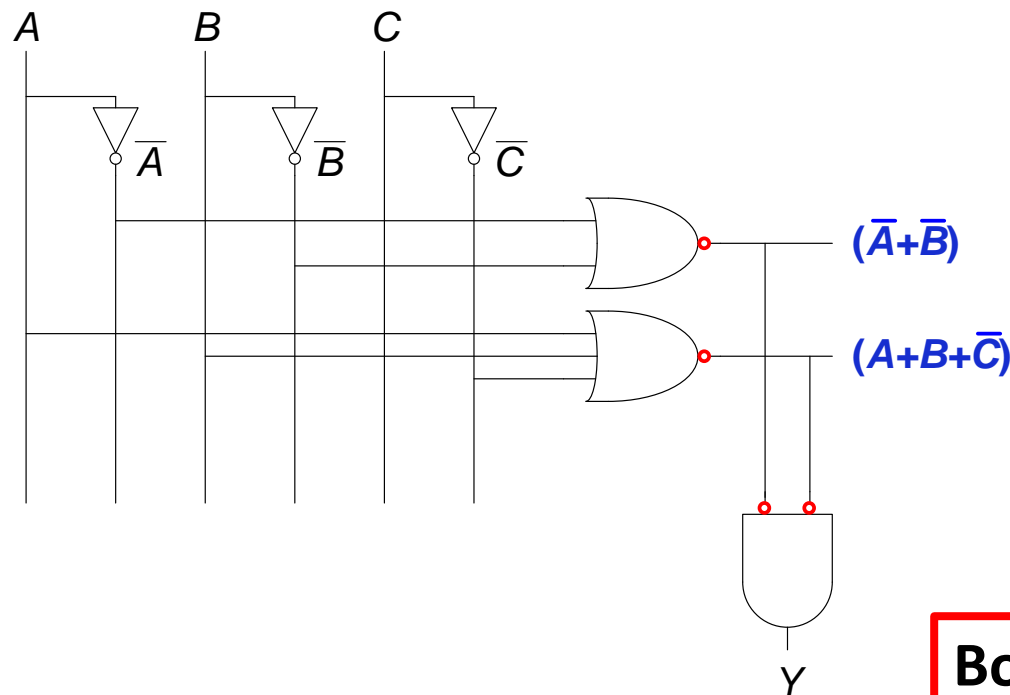- Two-level logic: **ORs** followed by **ANDs** → **NORs**
- Example: $Y = (\bar{A} + \bar{B})(A + B + \bar{C})$



Put **bubbles** on internal nodes.

Chapter 2: Combinational Logic

Bubble Pushing

De Morgan's Theorem

#	Theorem	Dual	Name
T12	$\overline{B \bullet C \bullet D \dots} = \bar{B} + \bar{C} + \bar{D} \dots$	$\overline{B + C + D \dots} = \bar{B} \bullet \bar{C} \bullet \bar{D} \dots$	De Morgan's Theorem

De Morgan's Theorem

Example D1:

$$\begin{aligned} Y &= \overline{A+BC} \\ &= \overline{A} \bullet \overline{\overline{BC}} \\ &= \overline{A} \bullet BC \\ &= \overline{A}BC \end{aligned}$$

- Work from the **outside in** (i.e., top bar, then down)
- Use **involution** when possible

De Morgan's Theorem

Example D2:

$$\begin{aligned} Y &= \overline{A+BC+\overline{A}\overline{B}} \\ &= \overline{A} \bullet \overline{\overline{BC}} \bullet \overline{\overline{A}\overline{B}} \\ &= \overline{A} \bullet BC \bullet (\overline{\overline{A}} + \overline{\overline{B}}) \\ &= \overline{A}BC \bullet (A + B) \\ &= \overline{A}BCA + \overline{A}BCB \\ &= \overline{A}BC \end{aligned}$$

- De Morgan **applies to**:
 - **Products** under a bar
 - **Sums** under a bar
- **Do not** try to apply DeMorgan's to a **mix of operations**

De Morgan's Theorem

Example D2:

$$Y = \overline{A + BC + \overline{A}\overline{B}}$$

$$= \overline{A} \cdot \overline{\overline{BC}} \cdot \overline{\overline{A}\overline{B}}$$

$$= \overline{A} \cdot BC \cdot (\overline{\overline{A}} + \overline{\overline{B}})$$

$$= \overline{A}BC \cdot (A + B)$$

$$= \overline{A}BCA + \overline{A}BCB$$

$$= \overline{A}BC$$


Don't forget these parentheses!

Remember:


$$\overline{\overline{A}\overline{B}} = (\overline{\overline{A}} + \overline{\overline{B}})$$

De Morgan's Theorem: Gates

 
- $Y = \overline{AB} = \overline{A} + \overline{B}$




NAND gate
two forms

 

 - $Y = \overline{A + B} = \overline{A} \cdot \overline{B}$




NOR gate
two forms

 

Bubble Pushing


- **Backward:**

- Body changes
- Adds bubbles to inputs

 


- **Forward:**

- Body changes
- Adds bubble to output

 


Bubble Pushing

 - What is the Boolean expression for this circuit?






Bubble Pushing Rules

 - Begin at output, then work toward inputs
- Push bubbles on final output back
- Draw gates in a form so bubbles cancel



Bubble Pushing Example

   


$$Y = \overline{A}\overline{B}C + \overline{D}$$

Chapter 2: Combinational Logic

X's and Z's, Oh My

Contention: X

 - **Contention:** circuit tries to drive output to 1 **and** 0 at the same time
 - Actual value somewhere in between 0 and 1
 - Could be 0, 1, or in forbidden zone
 - Might change with voltage, temperature, time, noise
 - Often causes excessive power dissipation




- X is also used for:
 - Uninitialized values
 - “Don’t care” values
- **Warnings:**
 - Contention or uninitialized outputs usually indicate a **bug**.
 - Look at the context to tell meaning

Floating: Z

- *Floating, high impedance, open, high Z*
- Floating output might be 0, 1, or somewhere in between
 - A voltmeter **won't** indicate whether a node is floating
 - But if you touch the node or your instructor walks over for a checkoff, it may change randomly

Tristate Buffer (High, Low, floating)

 


<i>E</i>	<i>A</i>	<i>Y</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

Tristate Buffers on Busses

Floating nodes are used in tristate busses

- Many different drivers
 - E.g., a microprocessor, a video controller, and an Ethernet controller all communicate with the memory system in a PC.
- Exactly one is active at once

 

Chapter 2: Combinational Logic

Karnaugh Maps

Karnaugh Maps (K-Maps)

- Boolean expressions can be minimized by combining terms
- K-maps minimize equations graphically
 - $PA + \overline{P}\overline{A} = P$

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y C	AB			
	00	01	11	10
0				
1				

Y C	AB			
	00	01	11	10
0	$\overline{A}\overline{B}\overline{C}$	$\overline{A}B\overline{C}$	$AB\overline{C}$	$A\overline{B}\overline{C}$
1	$\overline{A}\overline{B}C$	$\overline{A}BC$	ABC	$A\overline{B}C$

K-Map

- Circle 1's in adjacent squares
- In Boolean expression: include only literals whose true **and** complement forms are **not** in the circle

A	B	C	Y
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

Y C	AB			
	00	01	11	10
0	1	0	0	0
1	1	0	0	0

Y C	AB			
	00	01	11	10
0	$\bar{A}\bar{B}\bar{C}$	$\bar{A}B\bar{C}$	$AB\bar{C}$	$A\bar{B}\bar{C}$
1	$\bar{A}\bar{B}C$	$\bar{A}BC$	ABC	$A\bar{B}C$

$$Y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C = \bar{A}\bar{B}$$

3-Input K-Map

- Circle 1's in adjacent squares
- In Boolean expression: include only literals whose true **and** complement forms are ***not*** in the circle

Truth Table			
<i>A</i>	<i>B</i>	<i>C</i>	<i>Y</i>
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

		K-Map			
<i>Y</i>	<i>C</i>	<i>AB</i>			
		00	01	11	10
	0				
	1				

$Y =$

Some Definitions

- **Complement:** variable with a bar over it

$\bar{A}, \bar{B}, \bar{C}$

- **Literal:** variable or its complement

$A, \bar{A}, B, \bar{B}, C, \bar{C}$

- **Implicant:** product of literals

$AB\bar{C}, \bar{A}C, BC$

- **Prime implicant:** implicant corresponding to the **largest circle** in a K-map

K-Map Rules

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**


4-Input K-Map

<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>Y</i>
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

<i>Y</i> <i>CD</i>	<i>AB</i>			
	00	01	11	10
00				
01				
11				
10				

4-Input K-Map

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

 

$$Y = \bar{A}\bar{C} + \bar{A}BD + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{D}$$

Chapter 2: Combinational Logic

Karnaugh Maps with Don't Cares

K-Map Rules

- **Every 1 must be circled** at least once
- Each circle must span a **power of 2** (i.e. 1, 2, 4) squares in each direction
- Each circle must be as **large** as possible
- A circle may **wrap around the edges**
- Circle a “**don't care**” (X) **only if it helps minimize the equation**


K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

		AB			
Y	CD	00	01	11	10
Y	00				
	01				
	11				
	10				

K-Maps with Don't Cares

A	B	C	D	Y
0	0	0	0	1
0	0	0	1	0
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	X
0	1	1	0	1
0	1	1	1	1
1	0	0	0	1
1	0	0	1	1
1	0	1	0	X
1	0	1	1	X
1	1	0	0	X
1	1	0	1	X
1	1	1	0	X
1	1	1	1	X

 

$$Y = A + \bar{B}\bar{D} + C$$


Chapter 2: Combinational Logic

Combinational Building Blocks: Multiplexers

Multiplexer (*mux*)

- Selects between one of N inputs to connect to output
- **Select** input is $\log_2 N$ bits – control input
- Example:

2:1 *mux*

 

S	D_1	D_0	Y	S	Y
0	0	0	0	0	D_0
0	0	1	1	1	D_1
0	1	0	0		
0	1	1	1		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		


2:1 Multiplexer Implementations

- **Logic gates**

- Sum-of-products form


Y S	$D_0 D_1$		00	01	11	10
	0	1	0	0	1	1
1	0	1	0	1	1	0

$$Y = D_0 \bar{S} + D_1 S$$

 


- **Tristates**

 - Two tristate buffers
- Turn on exactly one to select the appropriate input




4:1 Multiplexer Implementations


2-Level Logic

 


Tristates

 

4:1 *mux* symbol

 

Hierarchical

 


Logic using Multiplexers

Using *mux* as a **lookup table**

<i>A</i>	<i>B</i>	<i>Y</i>
0	0	0
0	1	1
1	0	0
1	1	0

$$Y = \overline{A}B$$

 


Chapter 2: Combinational Logic

Combinational Building Blocks: Decoders


Decoders

 - N inputs, 2^N outputs
- **One-hot output:** only one output **HIGH** at once



A_1	A_0	Y_3	Y_2	Y_1	Y_0
0	0	0	0	0	1
0	1	0	0	1	0
1	0	0	1	0	0
1	1	1	0	0	0


Decoder Implementation

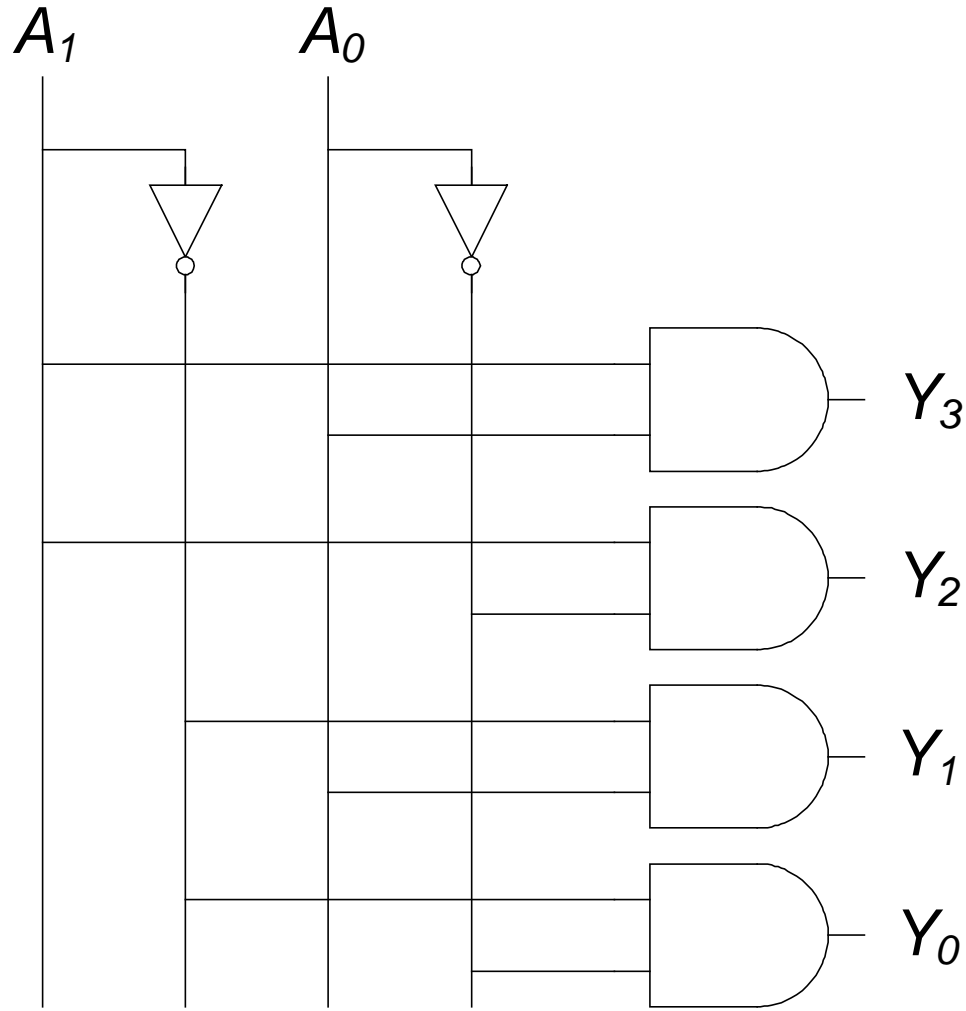

Logic Using Decoders

- Two-input XNOR using decoder

$$\begin{aligned} Y &= AB + \overline{A}\overline{B} \\ &= \overline{A \oplus B} \end{aligned}$$

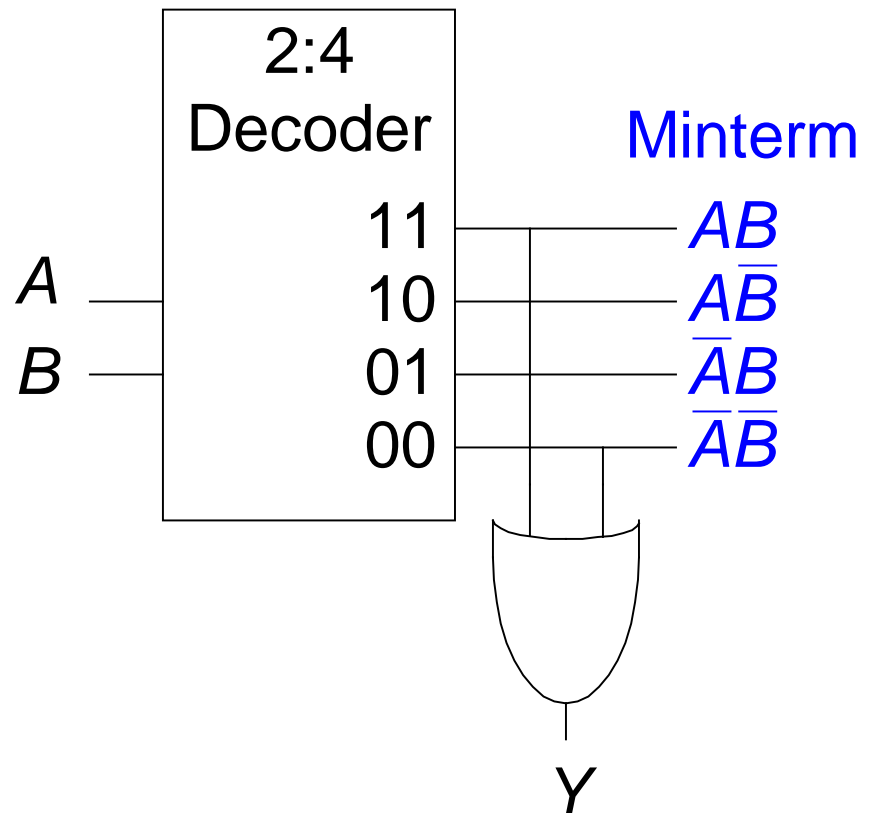


Chapter 2: Combinational Logic

Timing


Timing

 - **Delay:** time between input change and subsequent output change
- How to build fast circuits?



Propagation & Contamination Delay

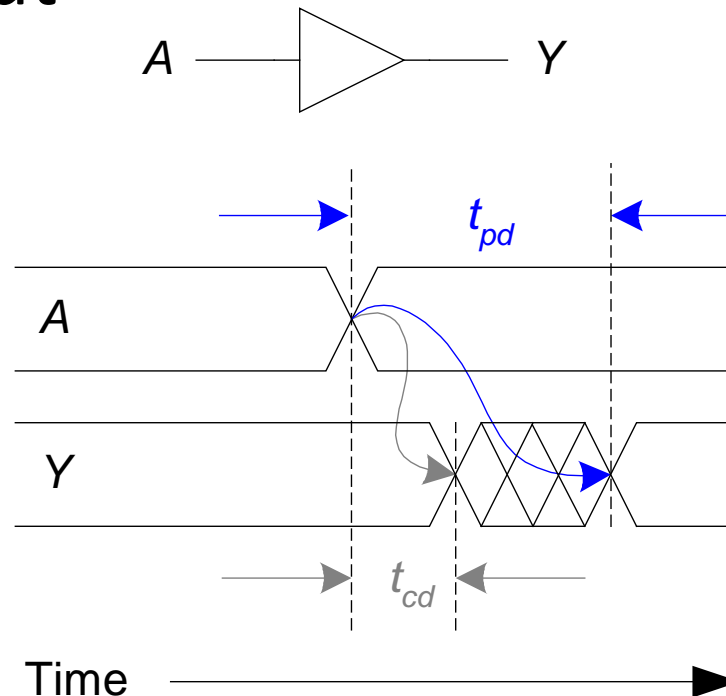
- **Propagation delay:** $t_{pd} = \mathbf{max}$ delay from input to output
- **Contamination delay:** $t_{cd} = \mathbf{min}$ delay from input to output



Propagation & Contamination Delay

- **Delay is caused by**
 - Capacitance charging and resistance in a circuit
 - Speed of light limitation
- **Reasons why t_{pd} and t_{cd} may be different:**
 - Different rising and falling delays
 - Multiple inputs and outputs, some of which are faster than others
 - Circuits slow down when hot and speed up when cold

Critical (Long) & Short Paths

 


Critical (Long) Path: $t_{pd} = 2t_{pd_AND} + t_{pd_OR}$ (max delay)

Short Path: $t_{cd} = t_{cd_AND}$ (min delay)

Glitches

- Def.: a single input change causes an output to change multiple times


 
- Q: What happens when $A = 0$, $C = 1$, B falls?



		AB			
		00	01	11	10
C	0	1	0	0	0
	1	1	1	1	0

$$Y = \bar{A}\bar{B} + BC$$

Glitches (cont.)

  


Fixing the Glitch

Y C \ AB	AB			
	00	01	11	10
0	1	0	0	0
1	1	1	1	0

$\bar{A}\bar{C}$

$$Y = \bar{A}\bar{B} + BC + \bar{A}C$$

.. covers the prime
implicant boundary

 

Why Understand Glitches?

- Because of **synchronous design** conventions (see Chapter 3), glitches don't cause problems.
- We **can't get rid of all glitches** – simultaneous transitions on multiple inputs can also cause glitches.
- It's important to **recognize** a glitch: in simulations or on oscilloscope.

About these Notes

Digital Design and Computer Architecture Lecture Notes

© 2021 Sarah Harris and David Harris

These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.