

Logic Circuit Design Homework #02			
Due date	Apr. 15 th , 2024	Instructor	Yoo, Younghwan
Student ID	202355517	Name	권민규

1. Write a Boolean equation in sum-of-products canonical form for each of the truth tables.

(a)				(b)				(c)			
A	B	Y		A	B	C	Y	A	B	C	Y
0	0	0		0	0	0	0	0	0	0	0
0	1	1		0	0	1	1	0	0	1	1
1	0	1		0	1	0	1	0	1	0	0
1	1	1		0	1	1	1	0	1	1	0
				1	0	0	1	1	0	0	0
				1	0	1	0	1	0	1	0
				1	1	0	1	1	1	0	1
				1	1	1	0	1	1	1	1

(a) $Y = \bar{A}B + A\bar{B} + \bar{A}\bar{B}$

(b) $Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC\bar{C}$

(c) $Y = \bar{A}\bar{B}C + AB\bar{C} + ABC$

2. Minimize each of the Boolean equations from Problem 1 using Boolean theorems. Show the minimization process.

(a)

$$\begin{aligned}
 Y &= \bar{A}B + A\bar{B} + \bar{A}\bar{B} \\
 &= \bar{A}(B + \bar{B}) + A\bar{B} \\
 &= \bar{A} + A\bar{B} \\
 &= (\bar{A} + A)(\bar{A} + \bar{B}) \\
 &= \bar{A} + \bar{B}
 \end{aligned}$$

(b)

$$\begin{aligned}
 Y &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + \bar{A}BC + A\bar{B}\bar{C} + ABC\bar{C} \\
 &= \bar{A}(\bar{B}C + B\bar{C} + BC) + A\bar{C}(\bar{B} + B) \\
 &= \bar{A}(\bar{B}C + BC + B\bar{C} + BC) + A\bar{C} \\
 &= \bar{A}((\bar{B} + B)C + B(\bar{C} + C)) + A\bar{C}
 \end{aligned}$$

$$= \bar{A}B + \bar{A}C + A\bar{C}$$


(c)

$$\begin{aligned} Y &= \bar{A}\bar{B}C + AB\bar{C} + ABC \\ &= \bar{A}\bar{B}C + AB(\bar{C} + C) \\ &= \bar{A}\bar{B}C + AB \end{aligned}$$

3. Simplify each of the following Boolean equations. Sketch a combinational circuit implementing the simplified equation.

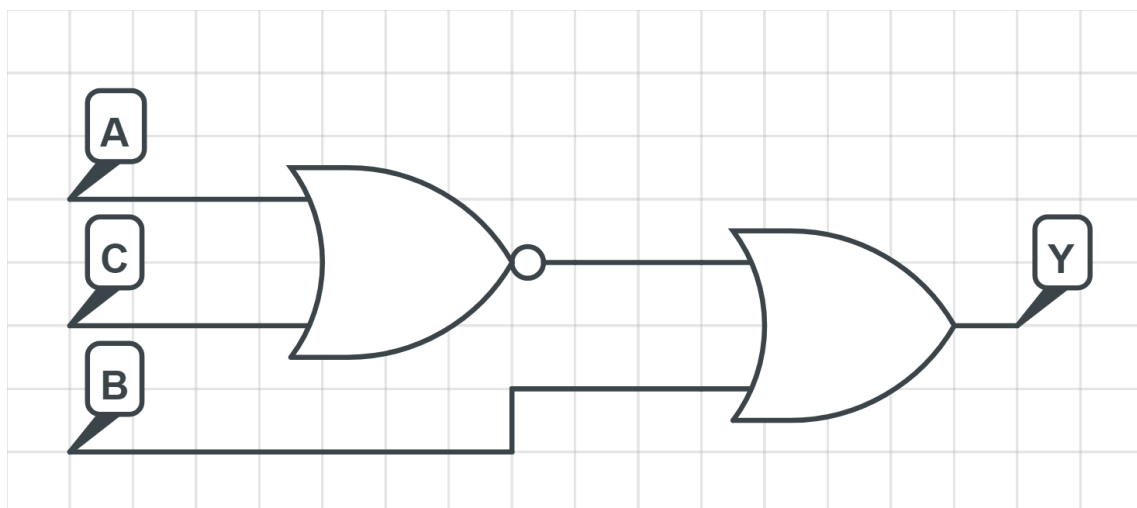
(a) $Y = BC + \bar{A}\bar{B}\bar{C} + B\bar{C}$

$$\begin{aligned} Y &= B(C + \bar{C}) + \bar{A}\bar{B}\bar{C} \\ &= B + \bar{A}B\bar{C} + \bar{A}\bar{B}\bar{C} \\ &= B + (B + \bar{B})\bar{A}\bar{C} \\ &= B + \bar{A}\bar{C} \end{aligned}$$




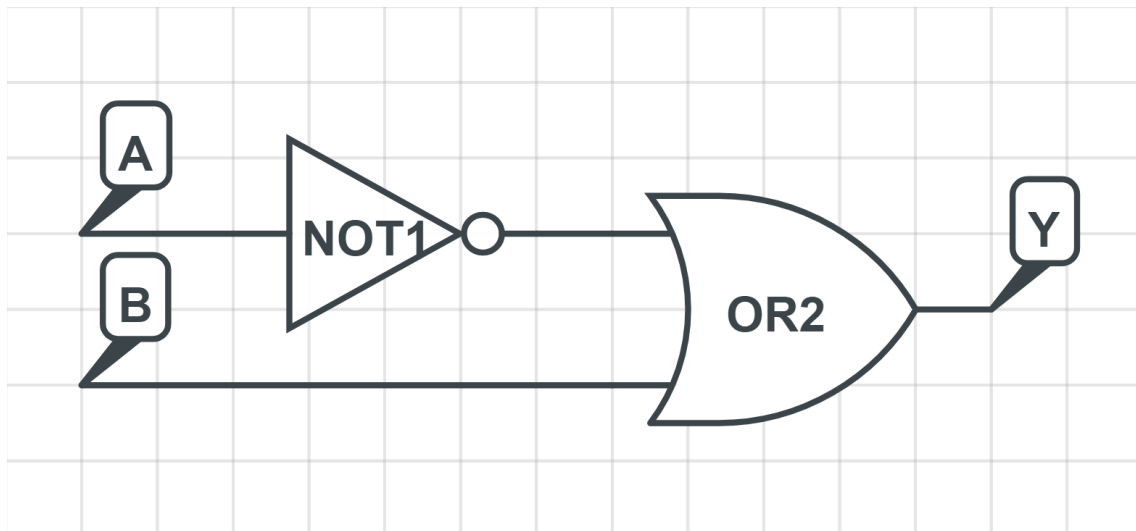(b) $Y = \overline{A + \bar{A}B + \bar{A}\bar{B}} + \overline{A + \bar{B}}$

$$\begin{aligned}
 Y &= \overline{A + \bar{A}(B + \bar{B})} + \bar{A}\bar{\bar{B}} \\
 &= \overline{A + \bar{A}} + \bar{A}B \\
 &= \bar{1} + \bar{A}B \\
 &= \bar{A}B
 \end{aligned}$$



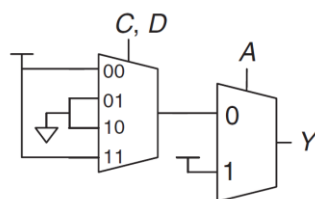4. Write a minimized Boolean equation for the function performed by the circuit in the figure below:



$$Y = A + CD + \bar{C}\bar{D}$$

