

Logic Circuit Design Homework #02			
Due date	Apr. 15 <sup>th</sup> , 2024	Instructor	Yoo, Younghwan
Student ID		Name	

1. Write a Boolean equation in sum-of-products canonical form for each of the truth tables.

(a)				(b)					(c)				
<i>A</i>	<i>B</i>		<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>		<i>Y</i>	<i>A</i>	<i>B</i>	<i>C</i>		<i>Y</i>
0	0		0	0	0	0		0	0	0	0		0
0	1		1	0	0	1		1	0	0	1		1
1	0		1	0	1	0		1	0	1	0		0
1	1		1	0	1	1		1	0	1	1		0
				1	0	0		1	1	0	0		0
				1	0	1		0	1	0	1		0
				1	1	0		1	1	1	0		1
				1	1	1		0	1	1	1		1

2. Minimize each of the Boolean equations from Problem 1 using Boolean theorems. Show the minimization process.

3. Simplify each of the following Boolean equations. Sketch a combinational circuit implementing the simplified equation.

(a)  $Y = BC + \bar{A}\bar{B}\bar{C} + B\bar{C}$

(b)  $Y = \overline{A + \bar{A}B + \bar{A}\bar{B}} + \overline{A + \bar{B}}$

4. Write a minimized Boolean equation for the function performed by the circuit in the figure below:

