

# Digital Design & Computer Architecture

Sarah Harris & David Harris

## Chapter 1: From Zero to One

*Modified by Younghwan Yoo, 2023*

# Chapter 1 :: Topics

- **The Art of Managing Complexity**
- **Number Systems**
  - Binary Numbers
  - Hexadecimal Numbers
  - Bits, Bytes, Nibbles
  - Addition
  - Signed Numbers
  - Extension
- **Logic Gates**
- **Logic Levels**
- **CMOS Transistors**
- **Transistor-Level Gate Design**
- **Power Consumption**

# Chapter 1: From Zero to One

## **The Art of Managing Complexity**


# The Art of Managing Complexity

- How do we design things that are too big to fit in one person's head at once?
- Abstraction
- Discipline
- The Three –y's
  - Hierarchy<sub>y</sub>
  - Modularity<sub>y</sub>
  - Regularity<sub>y</sub>
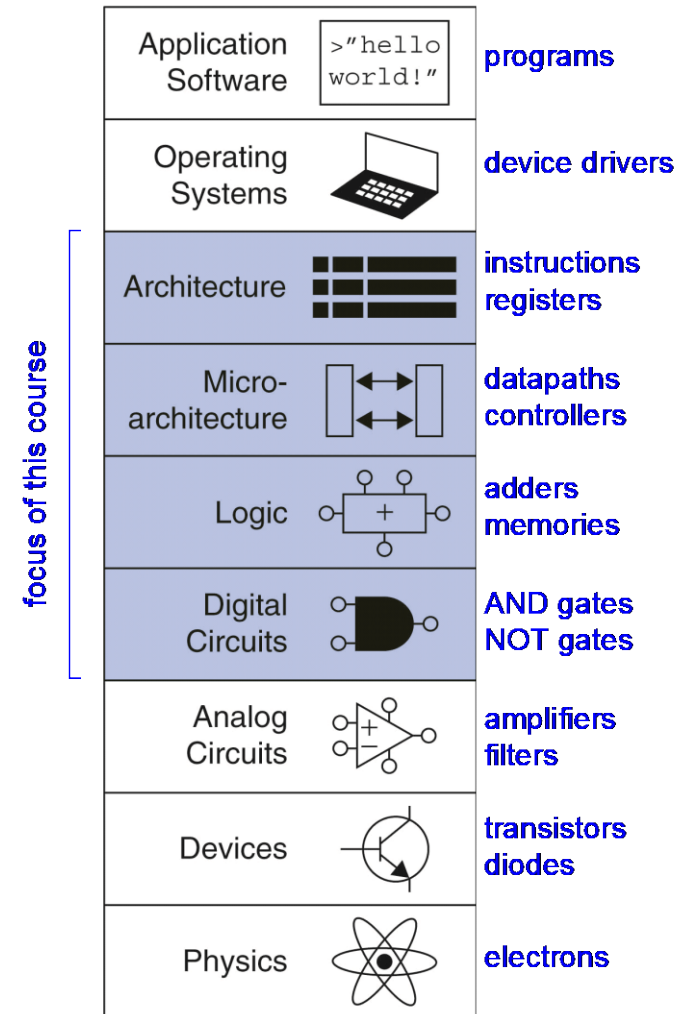
# Abstraction

Hiding details when they aren't important

- **Digital circuits:** logic gates converting analog voltages to 0 or 1
- **Logic design:** complex structures, e.g., adders and memories
- **Microarchitecture:** combining logic elements to execute instructions defined by *Architecture*
- **Architecture:** a set of instructions and registers that programmers use



# Discipline

- Intentionally restrict design choices
- Example: Digital discipline
  - Discrete voltages instead of continuous
  - Simpler to design than analog circuits – can build more sophisticated systems
  - Digital systems replacing analog predecessors: i.e., digital cameras, digital television, cell phones, CDs

# The Three -y's

- **Hierarchy**
  - A system divided into modules and submodules
- **Modularity**
  - Having well-defined functions and interfaces
- **Regularity**
  - Encouraging uniformity, so modules can be easily reused

# Digital Discipline: Binary Values

- **Two discrete values:**
  - 1's and 0's
  - 1, TRUE, HIGH
  - 0, FALSE, LOW
- **1 and 0:** voltage levels, rotating gears, fluid levels, etc.
- Digital circuits use voltage levels
  - 0: low voltage (GND)
  - 1: high voltage ( $V_{DD}$ )
- ***Bit: Binary digit***



# Chapter 1: From Zero to One

## **Number Systems: Binary Numbers**

# Number Systems

- Decimal numbers

Decimal numbers in digital systems mean any base 10 numbers, not just those with a decimal point.

1's column  
10's column  
100's column  
1000's column

$$5374_{10} = 5 \times 10^3 + 3 \times 10^2 + 7 \times 10^1 + 4 \times 10^0$$

five                      three                      seven                      four  
thousands              hundreds              tens                      ones

- Binary numbers

1's column  
2's column  
4's column  
8's column

$$1101_2 = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 = 13_{10}$$

one                      one                      no                      one  
eight                      four                      two                      one

# Counting in Binary

## Binary

## Decimal

0

0

1

1

10

2

11

3

100

4

101

5

...

# Powers of Two

- $2^0 = 1$

- $2^1 = 2$

- $2^2 = 4$

- $2^3 = 8$

- $2^4 = 16$

- $2^5 = 32$

- $2^6 = 64$

- $2^7 = 128$

- $2^8 = 256$

- $2^9 = 512$

- $2^{10} = 1024$

- $2^{11} = 2048$

- $2^{12} = 4096$

- $2^{13} = 8192$

- $2^{14} = 16384$

- $2^{15} = 32768$

**Handy to  
memorize**

# Number Conversion

- Binary to decimal conversion:
  - Convert  $10011_2$  to decimal
  - $16 \times 1 + 8 \times 0 + 4 \times 0 + 2 \times 1 + 1 \times 1 = 19_{10}$
- Decimal to binary conversion:
  - Convert  $47_{10}$  to binary
  - $32 \times 1 + 16 \times 0 + 8 \times 1 + 4 \times 1 + 2 \times 1 + 1 \times 1 = 101111_2$

# Decimal to Binary Conversion

- Two methods:
  - **Method 1:** Find the largest power of 2 that fits, subtract and repeat
  - **Method 2:** Repeatedly divide by 2, remainder goes in next most significant bit

# Decimal to Binary Conversion

$53_{10}$

**Method 1:** Find the largest power of 2 that fits, subtract and repeat

$$\begin{array}{rcl} 53_{10} & & 32 \times 1 \\ 53 - 32 = 21 & & 16 \times 1 \\ 21 - 16 = 5 & & 4 \times 1 \\ 5 - 4 = 1 & & 1 \times 1 \end{array} \quad = 110101_2$$

**Method 2:** Repeatedly divide by 2, remainder goes in next most significant bit

$$\begin{array}{rcl} 53_{10} = & 53/2 = 26 \text{ R}1 & \\ & 26/2 = 13 \text{ R}0 & \\ & 13/2 = 6 \text{ R}1 & \\ & 6/2 = 3 \text{ R}0 & \\ & 3/2 = 1 \text{ R}1 & \\ & 1/2 = 0 \text{ R}1 & \end{array} \quad = 110101_2$$

# Binary Values and Range

- ***N*-digit decimal number**
  - How many values?
  - Range?
  - Example: 3-digit decimal number:
    - 
    -
- ***N*-bit binary number**
  - How many values?
  - Range:
  - Example: 3-digit binary number:
    - 
    -



# Chapter 1: From Zero to One

## **Number Systems: Hexadecimal Numbers**

# Hexadecimal Numbers

- Base 16
- Shorthand for binary

Hex Digit	Decimal Equivalent	Binary Equivalent
0	0	0000
1	1	0001
2	2	0010
3	3	0011
4	4	0100
5	5	0101
6	6	0110
7	7	0111
8	8	1000
9	9	1001
A	10	1010
B	11	1011
C	12	1100
D	13	1101
E	14	1110
F	15	1111

# Hexadecimal to Binary Conversion

- Hexadecimal to binary conversion:
  - Convert  $4AF_{16}$  (also written  $0x4AF$ ) to binary
  -
- Hexadecimal to decimal conversion:
  - Convert  $4AF_{16}$  to decimal
  -

# Hexadecimal and Binary Prefixes

- Hard to write subscripts in text files
- Some programming languages uses prefixes
  - Hex: 0x
    - $0x23AB = 23AB_{16}$
  - Binary: 0b
    - $0b1101 = 1101_2$

# Chapter 1: From Zero to One

## **Number Systems: Bytes, Nibbles, & All That Jazz**

# Bits, Bytes, Nibbles...

- Byte: 8 bits
  - Represents one of \_\_\_\_\_ values
  - [\_\_, \_\_]
- Nibble: 4 bits
  - Represents one of \_\_\_\_\_ values
  - [\_\_, \_\_]

One binary digit is \_\_ bit

One hex digit is \_\_\_\_ bits or \_\_\_\_ nibble

Two hex digits make \_\_\_\_ byte

Most significant on left

Least significant on right

10010110

most significant bit      least significant bit

byte

10010110

nibble

CEBF9AD7

most significant byte      least significant byte

# Large Powers of Two

- $2^{10} = 1 \text{ kilo}$   $\approx 10^3$  (1024)
- $2^{20} = 1 \text{ mega}$   $\approx 10^6$  (1,048,576)
- $2^{30} = 1 \text{ giga}$   $\approx 10^9$  (1,073,741,824)
- $2^{40} = 1 \text{ tera}$   $\approx 10^{12}$
- $2^{50} = 1 \text{ peta}$   $\approx 10^{15}$
- $2^{60} = 1 \text{ exa}$   $\approx 10^{18}$

# Estimating Powers of Two

- What is the value of  $2^{24}$ ?
- How large of a value can a 32-bit integer variable represent?



# Chapter 1: From Zero to One

## **Number Systems: Addition**

# Addition

- Decimal

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 3734 \\ + 5168 \\ \hline 8902 \end{array}$$

- Binary

$$\begin{array}{r} 11 \leftarrow \text{carries} \\ 1011 \\ + 0011 \\ \hline 1110 \end{array}$$

# Binary Addition Examples

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1001 \\ + 0101 \\ \hline \end{array}$$

- Add the following 4-bit binary numbers

$$\begin{array}{r} 1011 \\ + 0110 \\ \hline \end{array}$$

# Overflow

- Digital systems operate on a **fixed number of bits**
- Overflow: when result is too big to fit in the available number of bits
- See previous example of  $11 + 6$

# Chapter 1: From Zero to One

## **Number Systems: Signed Numbers**

# Signed Binary Numbers

- Sign/Magnitude Numbers

Signed magnitude binary				Decimal
Sign	Magnitude			
0	1	0	1	+5
1	1	0	1	-5

- Two's Complement Numbers

0 0 0 1 0 1 0 0 → Binary number (+20)

1 1 1 0 1 0 1 1 → One's complement

1 1 1 0 1 0 1 1
+ 1
1 1 1 0 1 1 0 0

→ 2s complement (-20)

# Sign/Magnitude Numbers

- 1 sign bit,  $N-1$  magnitude bits
- Sign bit is the most significant (left-most) bit
  - Positive number: sign bit = 0
  - Negative number: sign bit = 1

$$A: \{a_{N-1}, a_{N-2}, \dots, a_2, a_1, a_0\}$$

$$A = (-1)^{a_{N-1}} \sum_{i=0}^{N-2} a_i 2^i$$

- Example, 4-bit sign/mag representations of  $\pm 6$ :
  - +6 =
  - 6 =
- Range of an  $N$ -bit sign/magnitude number:

# Sign/Magnitude Numbers

## Problems:

- Addition doesn't work, for example  $-6 + 6$ :

$$\begin{array}{r} 1110 \\ + 0110 \\ \hline 10100 \text{ (wrong!)} \end{array}$$

- Two representations of 0 ( $\pm 0$ ):

1000

0000



# Two's Complement Numbers

- Don't have same problems as sign/magnitude numbers:
  - **Addition works**
  - **Single representation for 0**

0 0 0 1 0 1 0 0 → Binary number (+20)

1 1 1 0 1 0 1 1 → One's complement

1 1 1 0 1 0 1 1
+ 1
1 1 1 0 1 1 0 0

→ 2s complement (-20)

# Two's Complement Numbers

- msb has weight of  $-2^{N-1}$

$$A = a_{N-1}(-2^{N-1}) + \sum_{i=0}^{N-2} a_i 2^i$$

- Most positive 4-bit number:
- Most negative 4-bit number:
- The most significant bit still indicates the sign (1 = negative, 0 = positive)
- Range of an  $N$ -bit two's complement number:

# Reversing the Sign

- **How to reverse the sign** of a two's complement number
  1. Invert the bits
  2. Add 1
- **Example:** Reverse the sign of  $3_{10} = 0011_2$ 
  - 1.
  - 2.

Historically, this reversing the sign method has been called: “Taking the Two’s complement”. But this terminology can be confusing, so we instead we call it “reversing the sign”.

# Two's Complement Examples

- Reverse the sign of  $6_{10} = 0110_2$ 
  - 1.
  - 2.
- What is the decimal value of the two's complement number  $1001_2$ ?
  - 1.
  - 2.

# Two's Complement Addition

- Add  $6 + (-6)$  using two's complement numbers

$$\begin{array}{r} 0110 \\ + 1010 \\ \hline \end{array}$$

- Add  $-2 + 3$  using two's complement numbers

$$\begin{array}{r} 1110 \\ + 0011 \\ \hline \end{array}$$

# Subtraction


- Subtract a 2's complement number by reversing the sign and adding.
- Reverse sign by taking 2's complement
- Ex:  $3 - 5 = 3 + (-5)$

$$\begin{array}{r} 0011 \quad 3 \\ + 1011 \quad -5 \\ \hline 1110 \quad -2 \end{array}$$

# Number System Comparison

Number System	Range
Unsigned	$[0, 2^N-1]$
Sign/Magnitude	$[-(2^{N-1}-1), 2^{N-1}-1]$
Two's Complement	$[-2^{N-1}, 2^{N-1}-1]$

For example, 4-bit representation:

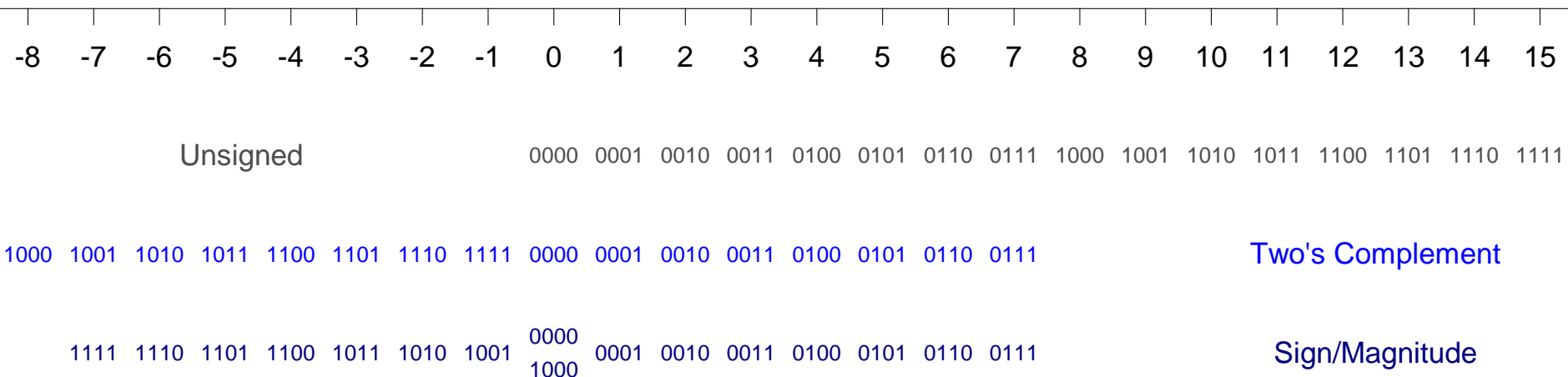

# Chapter 1: From Zero to One

## **Number Systems: Extension**



# Increasing Bit Width

**Extend number from  $N$  to  $M$  bits ( $M > N$ ) :**

- **Sign-extension** for 2's complement numbers
- **Zero-extension** for unsigned numbers

# Sign-Extension

- Sign bit copied to msb's
- Number value is same
- **Example 1:**
  - 4-bit representation of 3 = 0011
  - 8-bit sign-extended value: 00000011
- **Example 2:**
  - 4-bit representation of -5 = 1011
  - 8-bit sign-extended value: 11111011

# Zero-Extension

- Zeros copied to msb's
- Value changes for negative numbers

- **Example 1:**

- 4-bit value =  $0011 = 3_{10}$
- 8-bit zero-extended value: **0000**0011 =  $3_{10}$

- **Example 2:**

- 4-bit value =  $1011 = -5_{10}$
- 8-bit zero-extended value: **0000**1011 =  $11_{10}$

# Chapter 1: From Zero to One


## **Logic Gates**

# Logic Gates

- **Perform logic functions:**
  - inversion (NOT), AND, OR, NAND, NOR, etc.
- **Single-input:**
  - NOT gate, buffer
- **Two-input:**
  - AND, OR, XOR, NAND, NOR, XNOR
- **Multiple-input**

# Single-Input Logic Gates


**NOT**

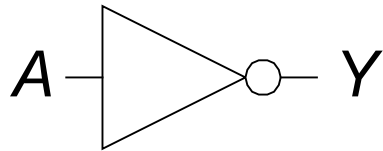

$$Y = \overline{A}$$

A	Y
0	1
1	0

**BUF**

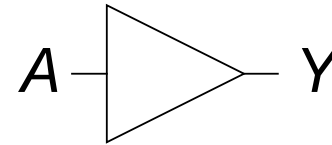


$$Y = A$$

A	Y
0	0
1	1

# Two-Input Logic Gates


## AND

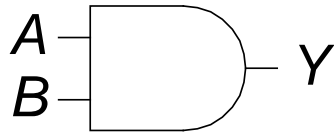

$$Y = AB$$

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

## OR

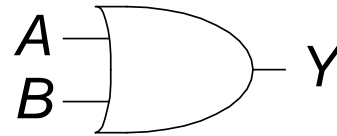


$$Y = A + B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	1

# More Two-Input Logic Gates


## XOR

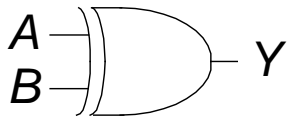

$$Y = A \oplus B$$

A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0


## NAND

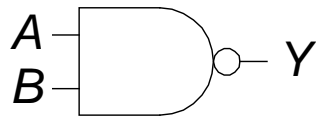

$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0


## NOR

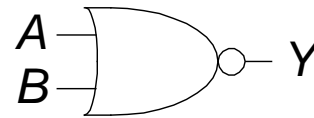

$$Y = \overline{A + B}$$

A	B	Y
0	0	1
0	1	0
1	0	0
1	1	0

## XNOR

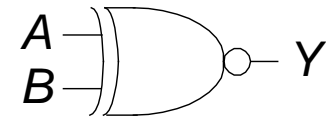

$$Y = \overline{A \oplus B}$$


A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

... called *equality gate*  
because it is TRUE  
when inputs are equal



# Multiple-Input Logic Gates


## NOR3

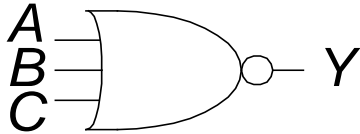

$$Y = \overline{A+B+C}$$

A	B	C	Y
0	0	0	1
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

## AND3

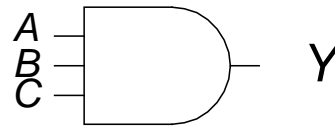


$$Y = ABC$$

A	B	C	Y
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	


Truth table rows  
are listed in  
binary order.

# Multiple-Input XOR

- Odd parity

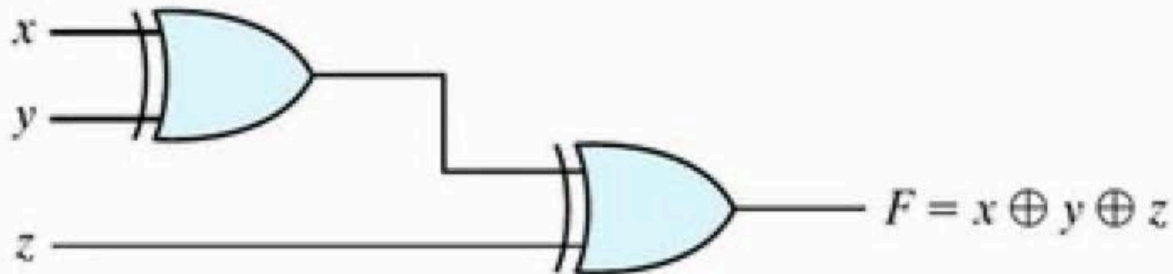

(a) Using 2-input gates

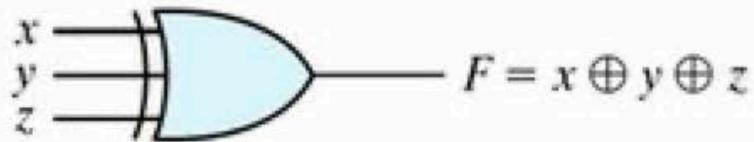


(b) 3-input gate

$x$	$y$	$z$	$F$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

(c) Truth table
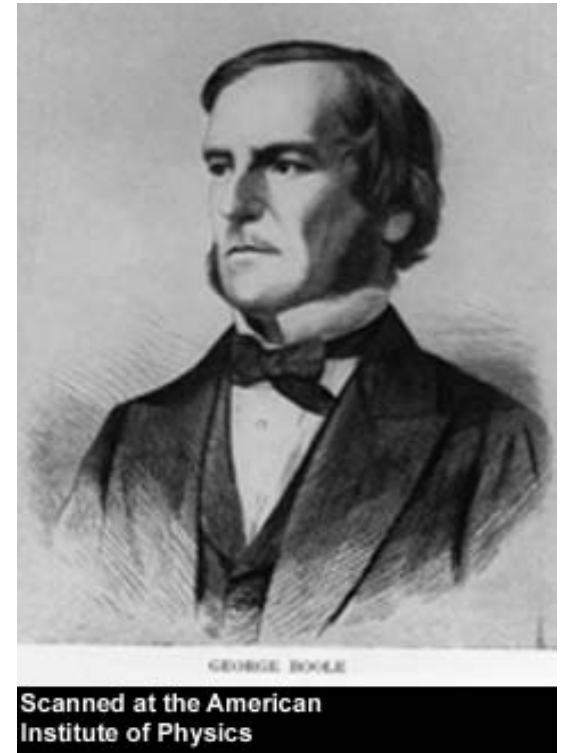
# George Boole, 1815-1864

- Born to working class parents
- Taught himself mathematics and joined the faculty of Queen's College in Ireland
- Wrote *An Investigation of the Laws of Thought* (1854)
- Introduced binary variables
- Introduced the three fundamental logic operations: AND, OR, and NOT



# Chapter 1: From Zero to One

## **Logic Levels**

# Logic Levels


- Discrete voltages represent 1 and 0
- For example:
  - 0 = *ground* (GND) or 0 volts
  - 1 =  $V_{DD}$  or 5 volts
- What about 4.99 volts? Is that a 0 or a 1?
- What about 3.2 volts?

# Logic Levels

- *Range* of voltages for 1 and 0
- Different ranges for inputs and outputs to allow for *noise*
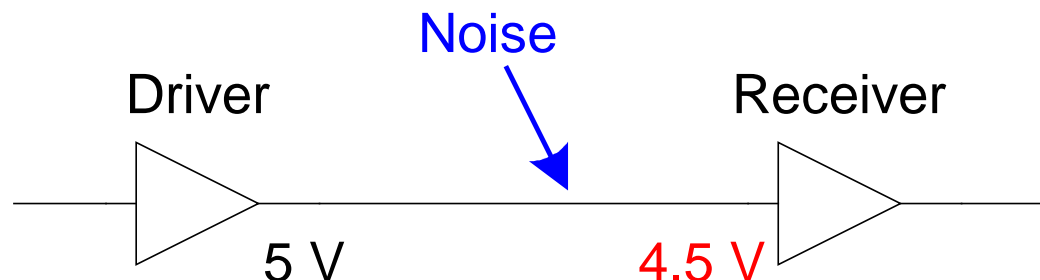
# What is Noise?

- **Anything that degrades the signal**
  - E.g., resistance, power supply noise, coupling to neighboring wires, etc.
- **Example:** a gate (driver) outputs 5 V but, because of resistance in a long wire, receiver gets 4.5 V




# The Static Discipline


- With logically valid inputs, every circuit element must produce logically valid outputs
- Use limited ranges of voltages to represent discrete values



# Noise Margins

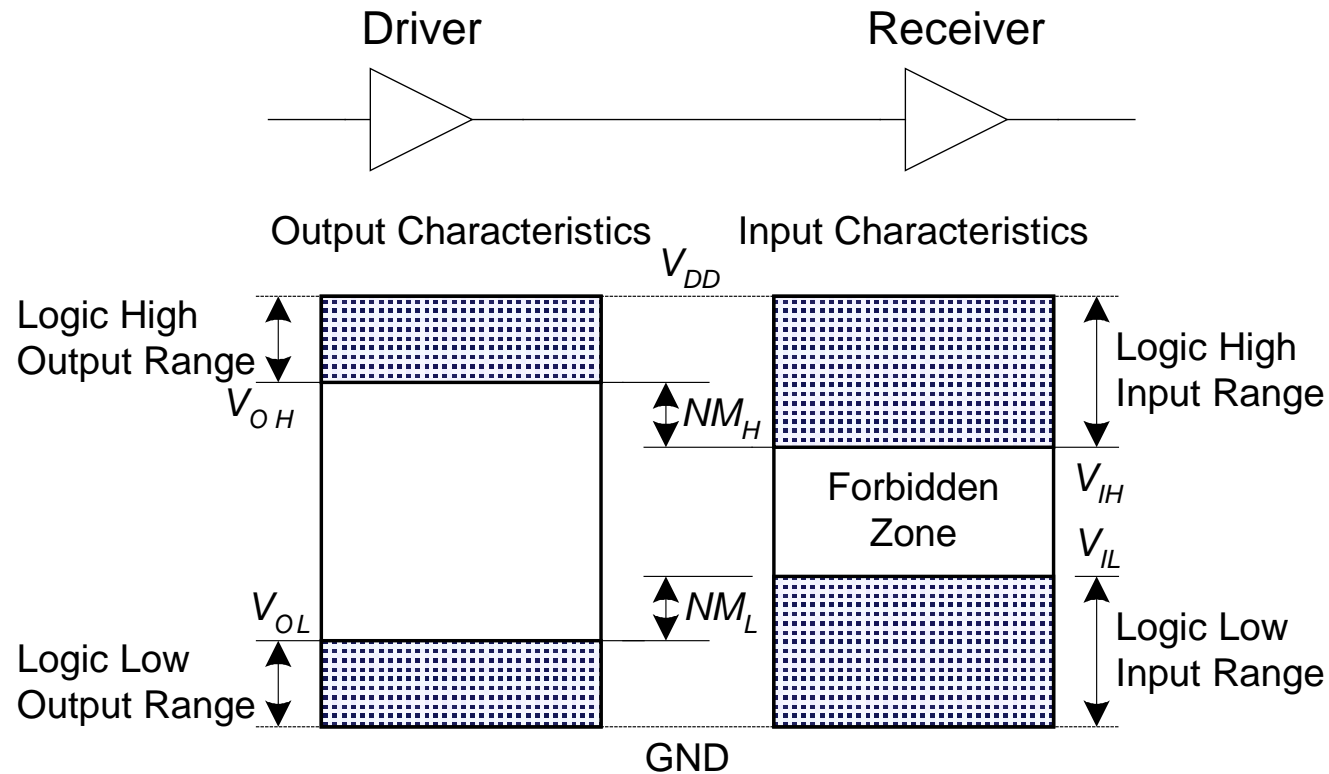

# Noise Margins

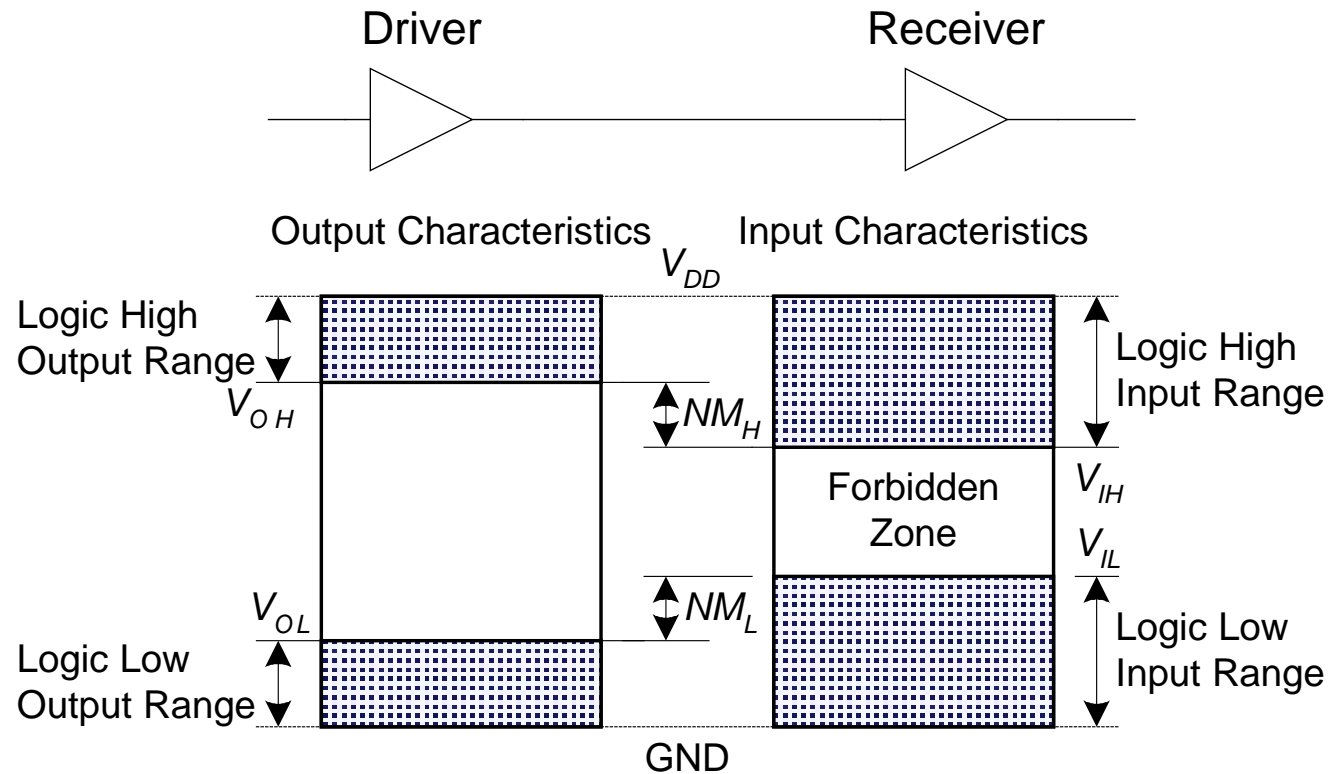


**High Noise Margin:**  $NM_H =$

**Low Noise Margin:**  $NM_L =$


# DC Transfer Characteristics

## Ideal Buffer:

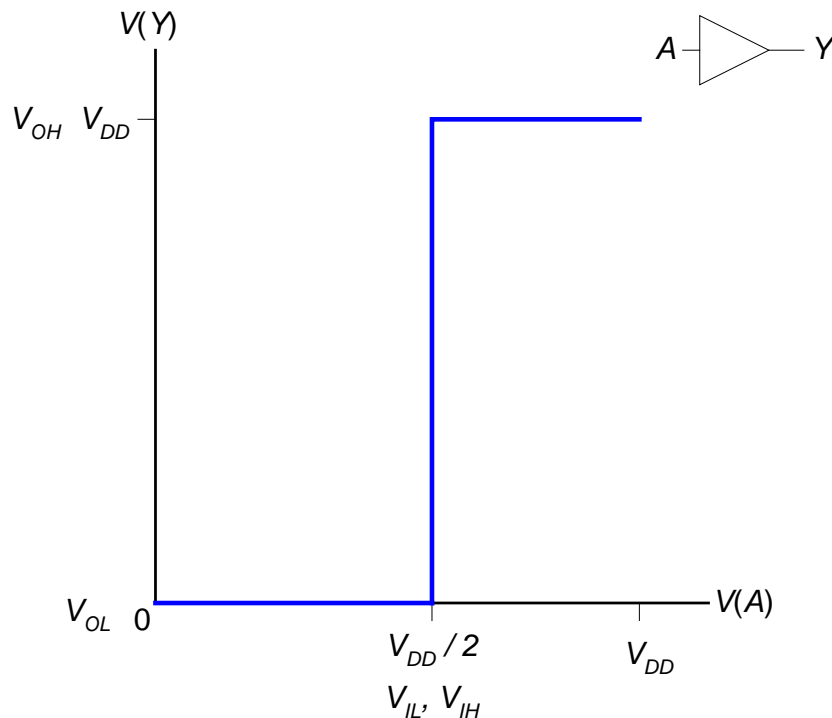




$$NM_H = NM_L = V_{DD}/2$$

## Real Buffer:

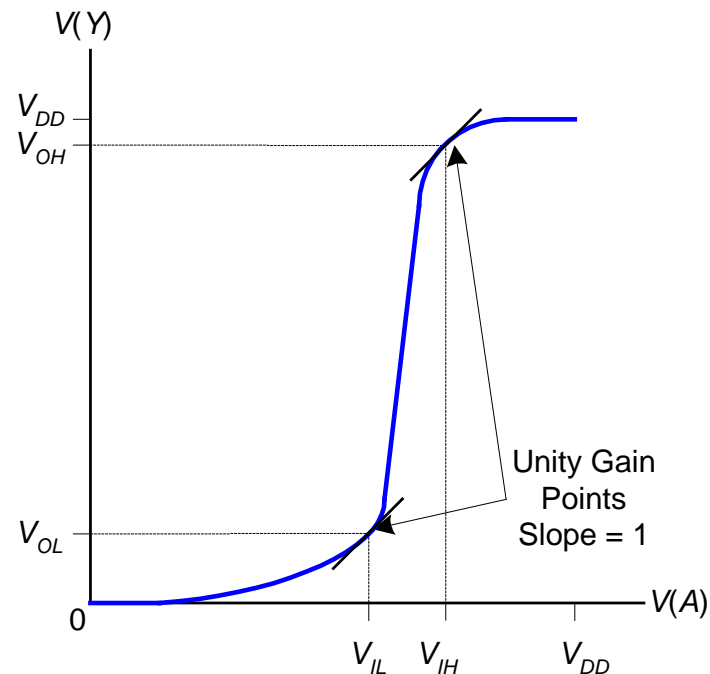

$$NM_H, NM_L < V_{DD}/2$$

# DC Transfer Characteristics

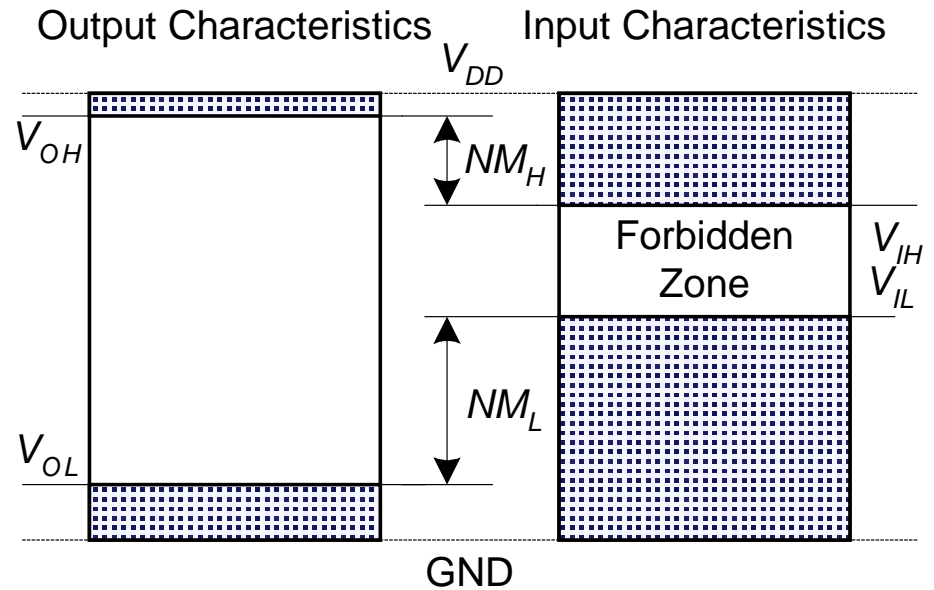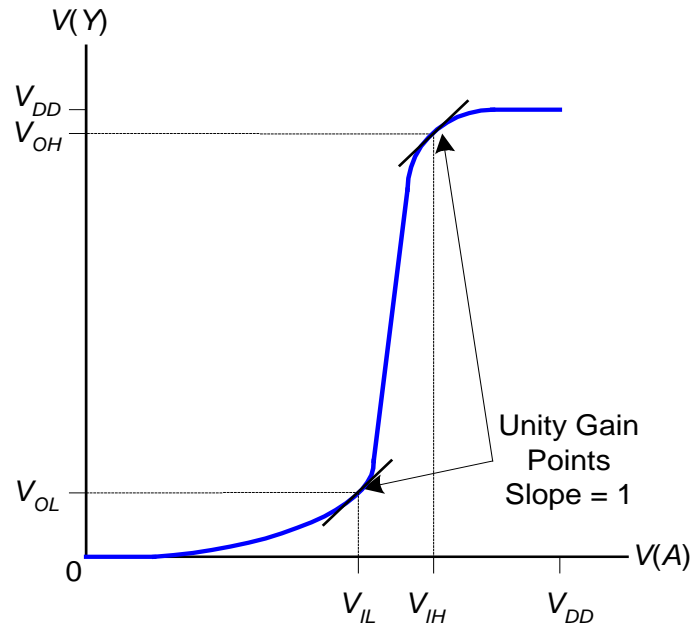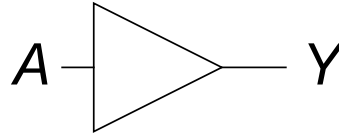

# $V_{DD}$ Scaling

- In 1970's and 1980's,  $V_{DD} = 5\text{ V}$
- $V_{DD}$  has dropped
  - Avoid frying tiny transistors
  - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
  - Be careful connecting chips with different supply voltages

# $V_{DD}$ Scaling

- In 1970's and 1980's,  $V_{DD} = 5\text{ V}$
- $V_{DD}$  has dropped
  - Avoid frying tiny transistors
  - Save power
- 3.3 V, 2.5 V, 1.8 V, 1.5 V, 1.2 V, 1.0 V, ...
  - Be careful connecting chips with different supply voltages

# Logic Family Examples

Logic Family	$V_{DD}$	$V_{IL}$	$V_{IH}$	$V_{OL}$	$V_{OH}$
<b>TTL</b>	5 (4.75 - 5.25)	0.8	2.0	0.4	2.4
<b>CMOS</b>	5 (4.5 - 6)	1.35	3.15	0.33	3.84
<b>LVTTTL</b>	3.3 (3 - 3.6)	0.8	2.0	0.4	2.4
<b>LVC MOS</b>	3.3 (3 - 3.6)	0.9	1.8	0.36	2.7

- Transistor–Transistor Logic (TTL)
- Complementary Metal–Oxide–Semiconductor (CMOS)


# Chapter 1: From Zero to One

## **CMOS Transistors**




# Switch

- AND operation:  
 $1 \times 1 = 1$

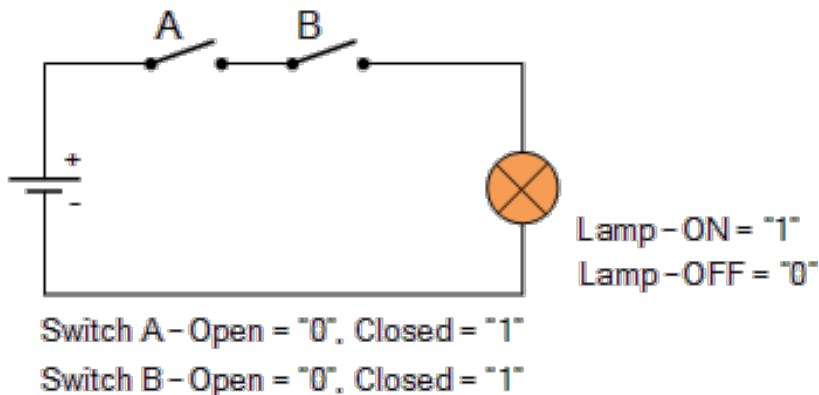


- OR operation:  
 $0 + 0 = 0$

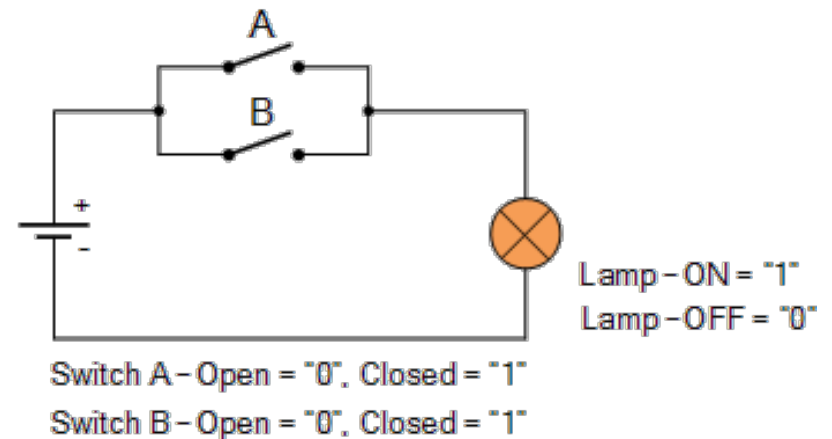

*How can we make electronically controlled switches?*
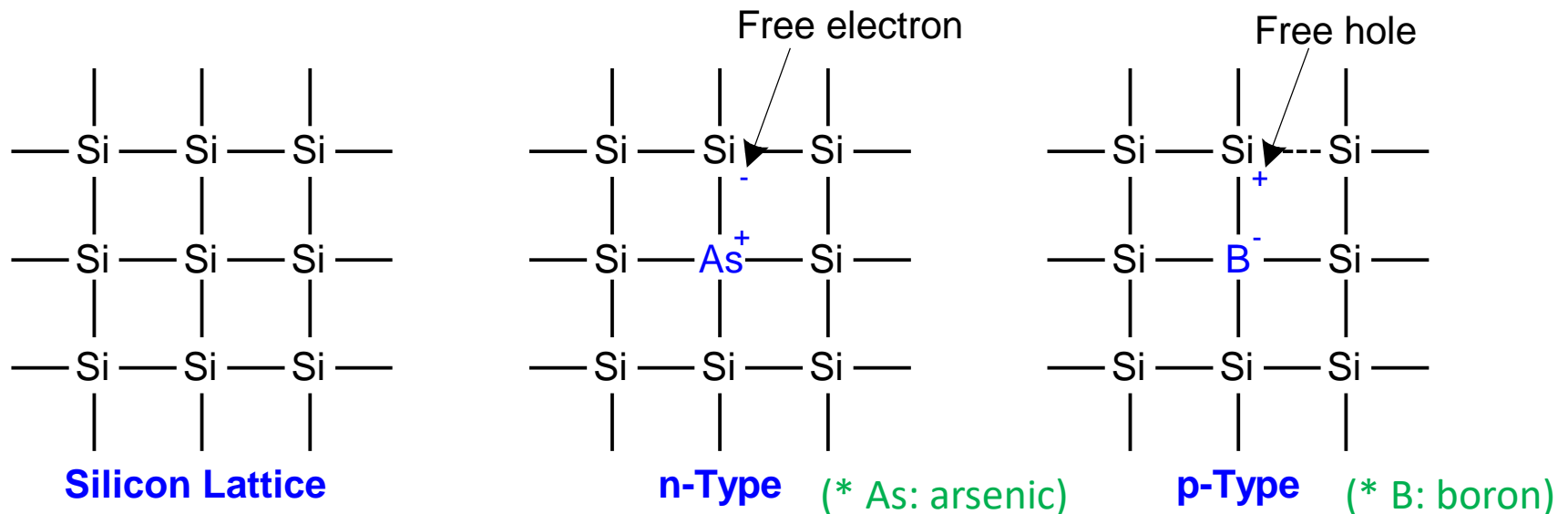
# Silicon


- Pure silicon is a poor conductor (no free charges)
- Doped silicon is a good conductor (free charges)
  - n-type (free **n**egative charges, electrons)
  - p-type (free **p**ositive charges, holes)



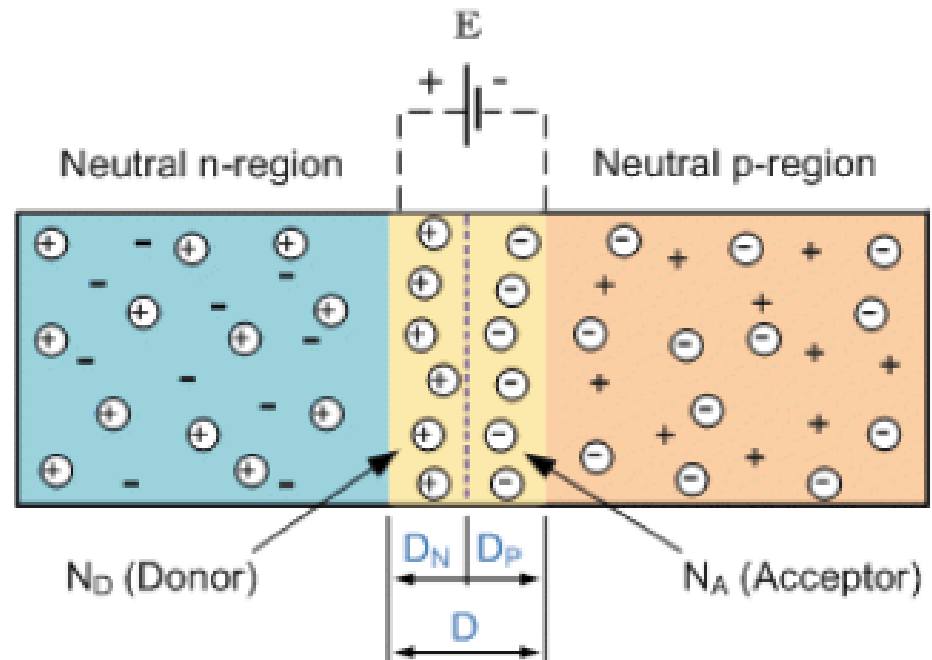
# Semiconductor

- **Feature**

- Insulator at low temperature
- Conductor if energy is given to make electrons jump from valence band to conduction band





# Semiconductor

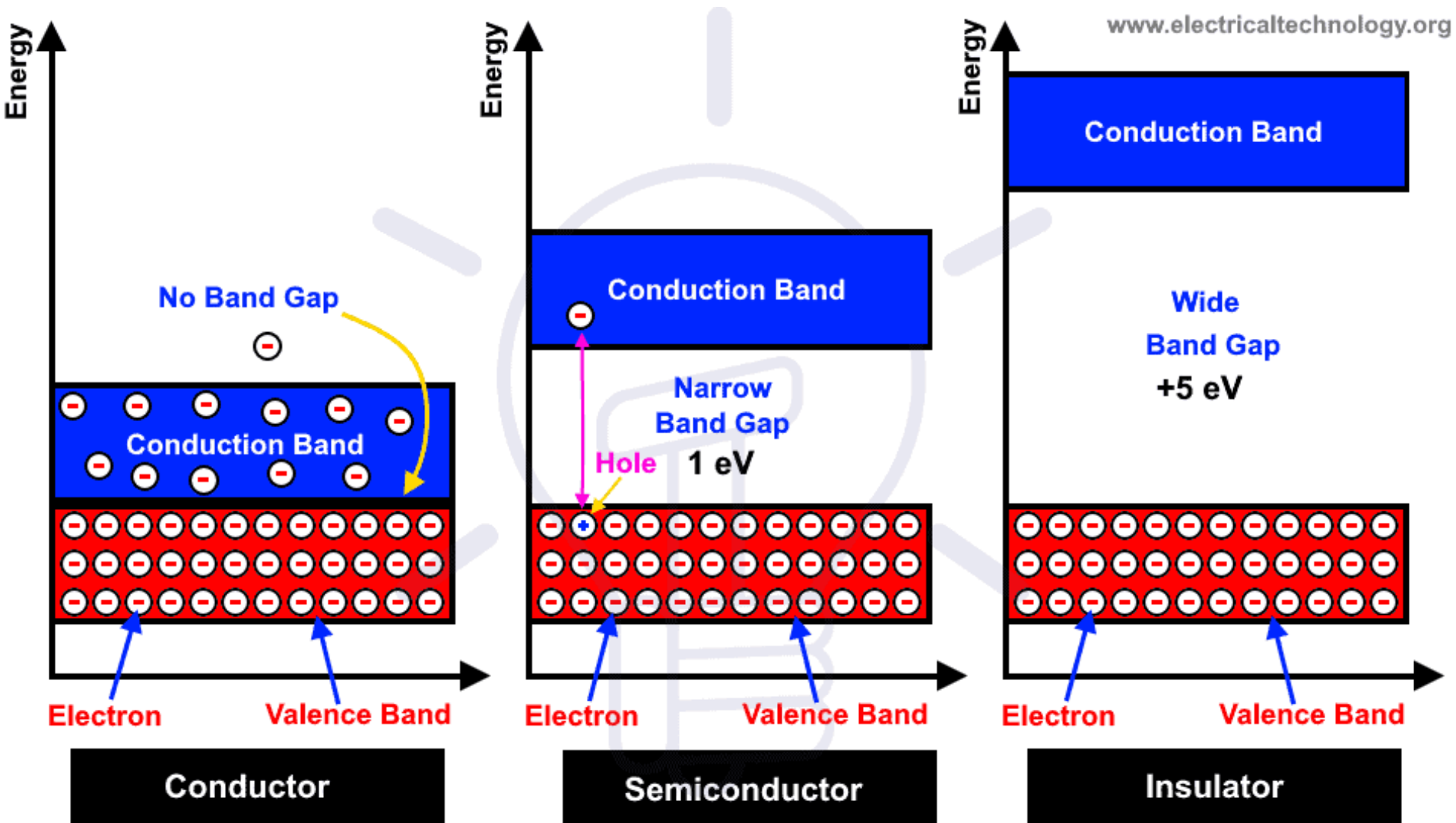

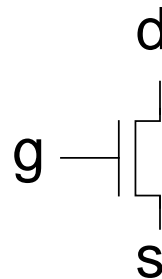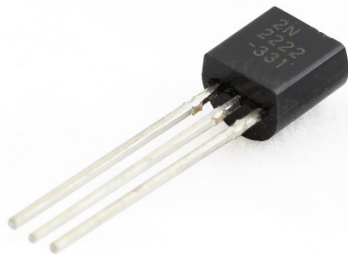
# Transistors


- Transistors built from silicon, a semiconductor
- Logic gates built from transistors
- 3-ported voltage-controlled switch
  - 2 ports connected depending on voltage of 3<sup>rd</sup> port
  - d and s are connected (ON) when  $g$  is 1



$g = 0$

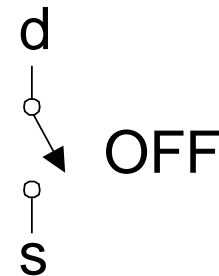


$g = 1$

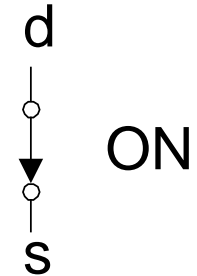


# Logic Gates with Transistors


- AND gate

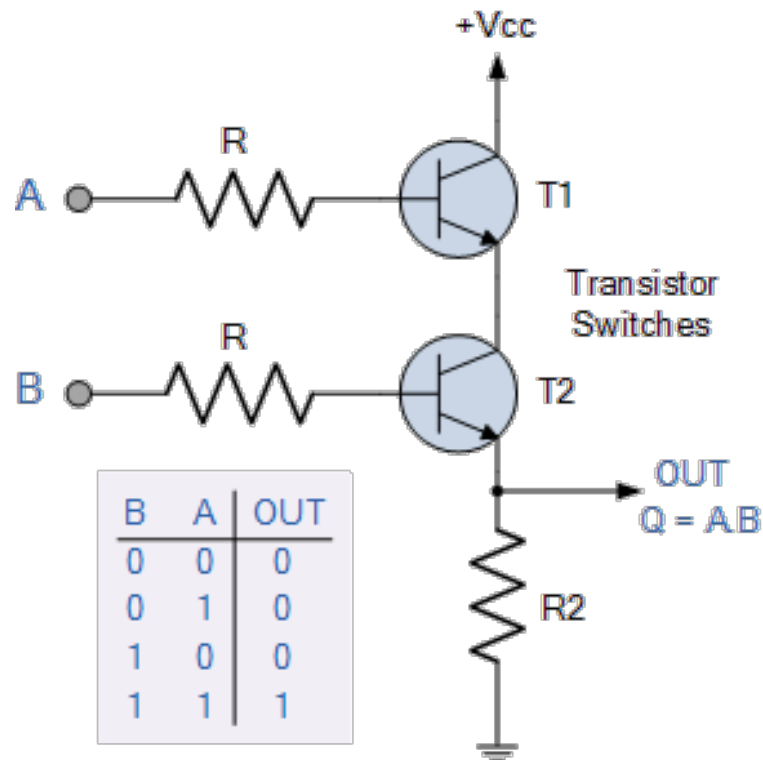


- OR gate

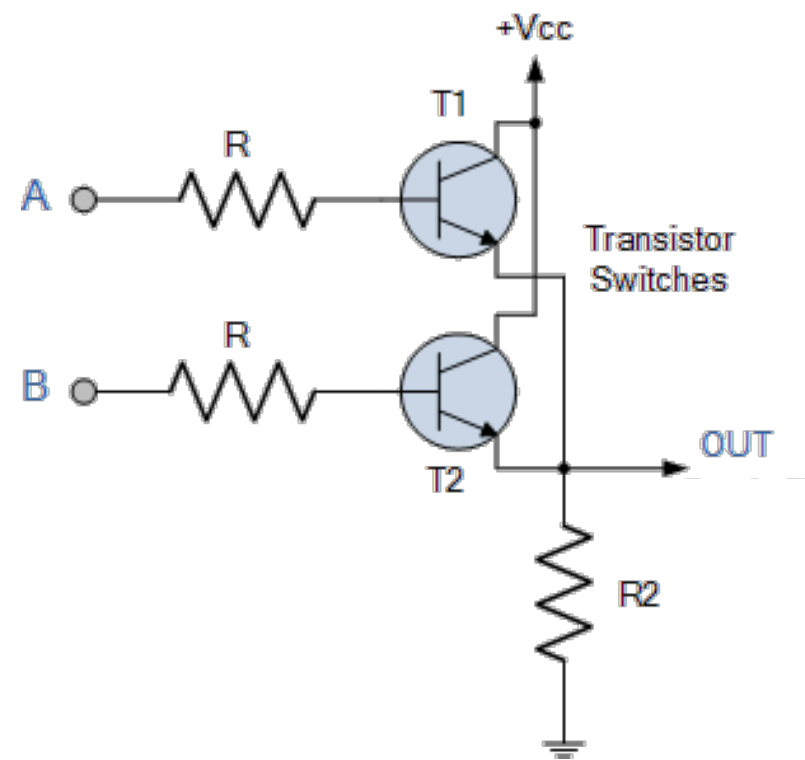


# Logic Gates with Transistors

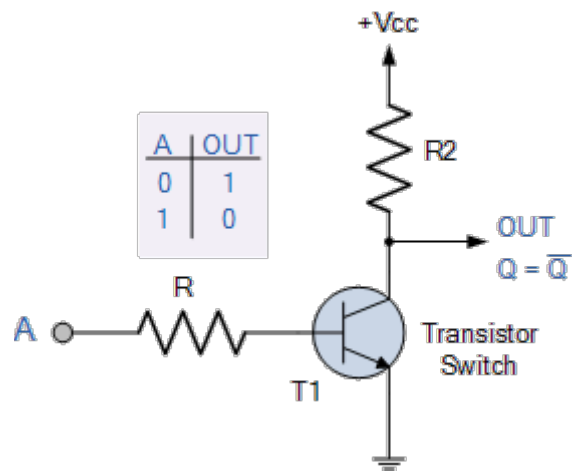

NOT

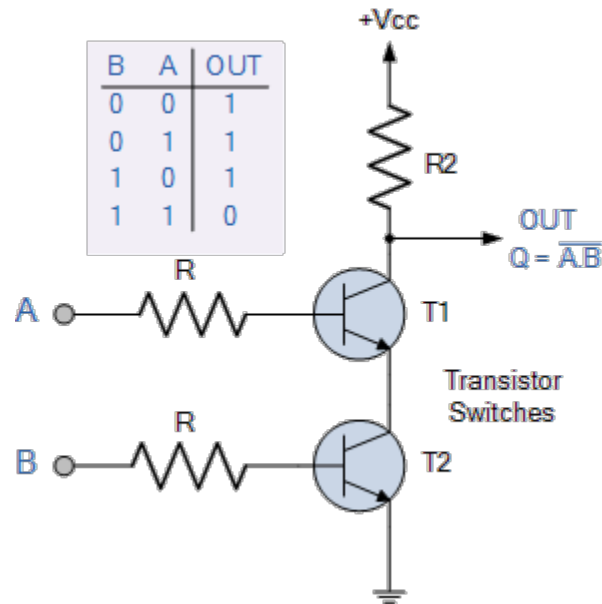



NAND

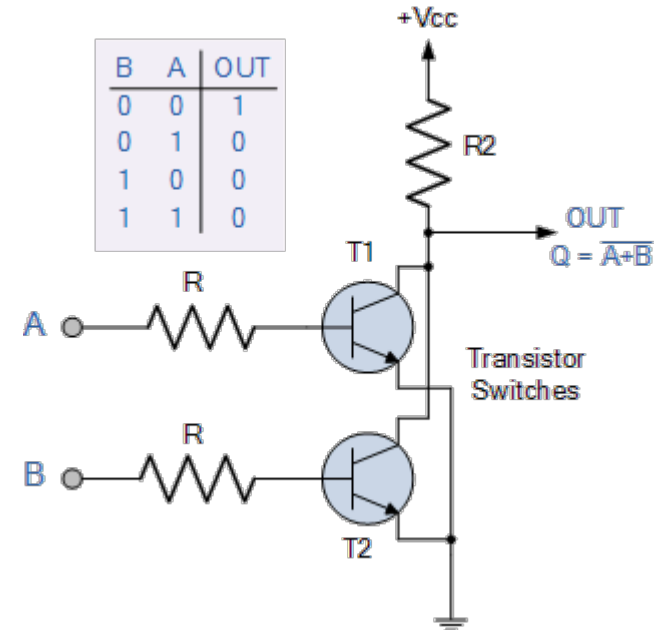

NOR
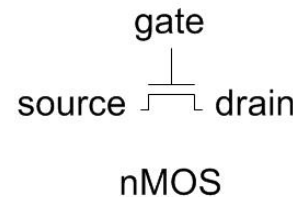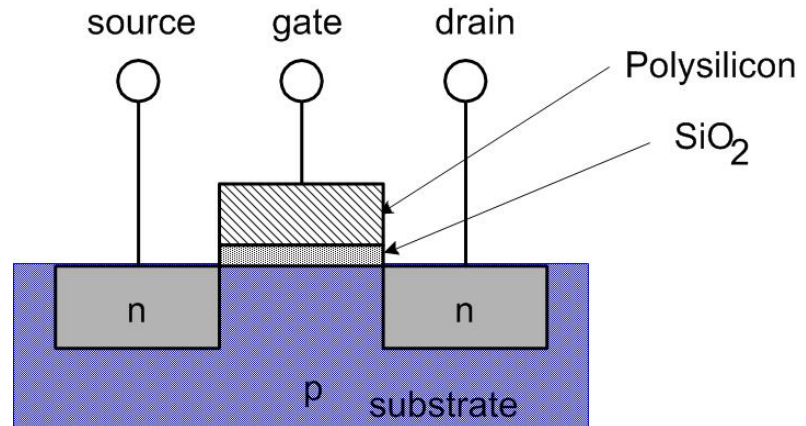
# MOS Transistors

- **Metal oxide silicon (MOS) transistors:**
  - Polysilicon (used to be **metal**) gate
  - **Oxide** (silicon dioxide) insulator
  - Doped **silicon**






# Transistors: nMOS

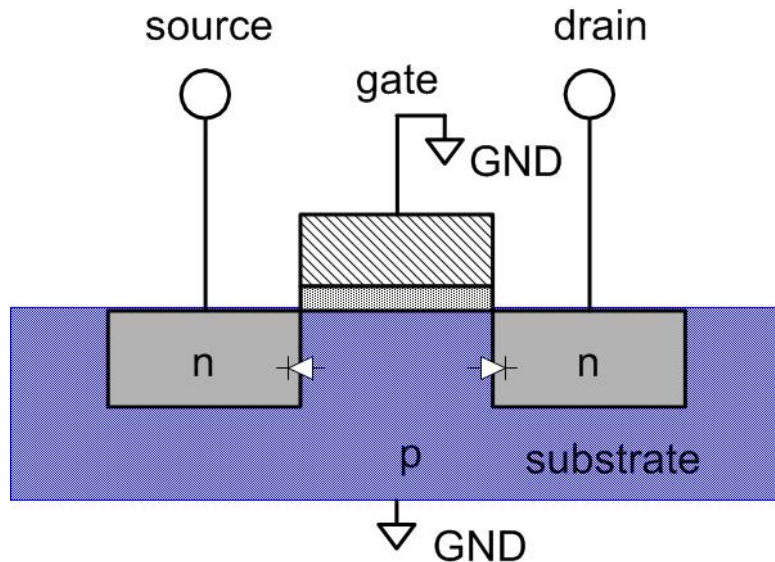
**Gate = 0**

**OFF** (no connection between source and drain)



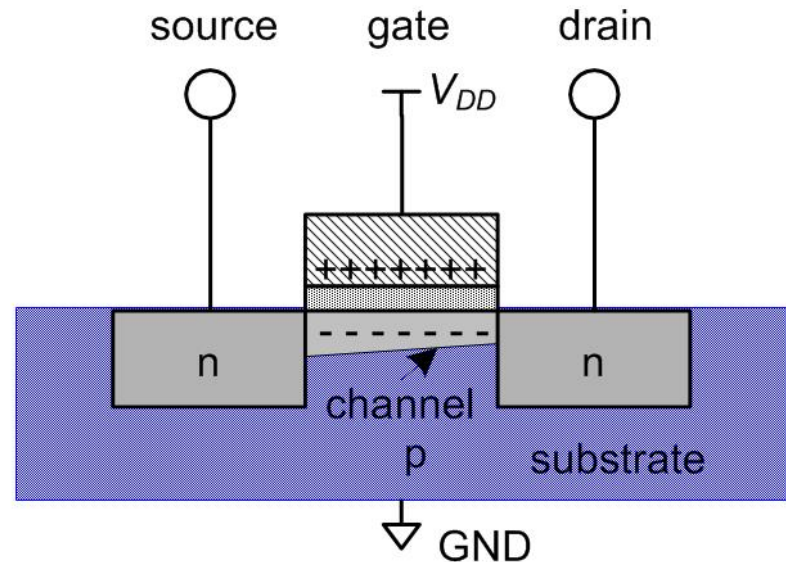**Gate = 1**


**ON** (channel between source and drain)



# Transistors: pMOS

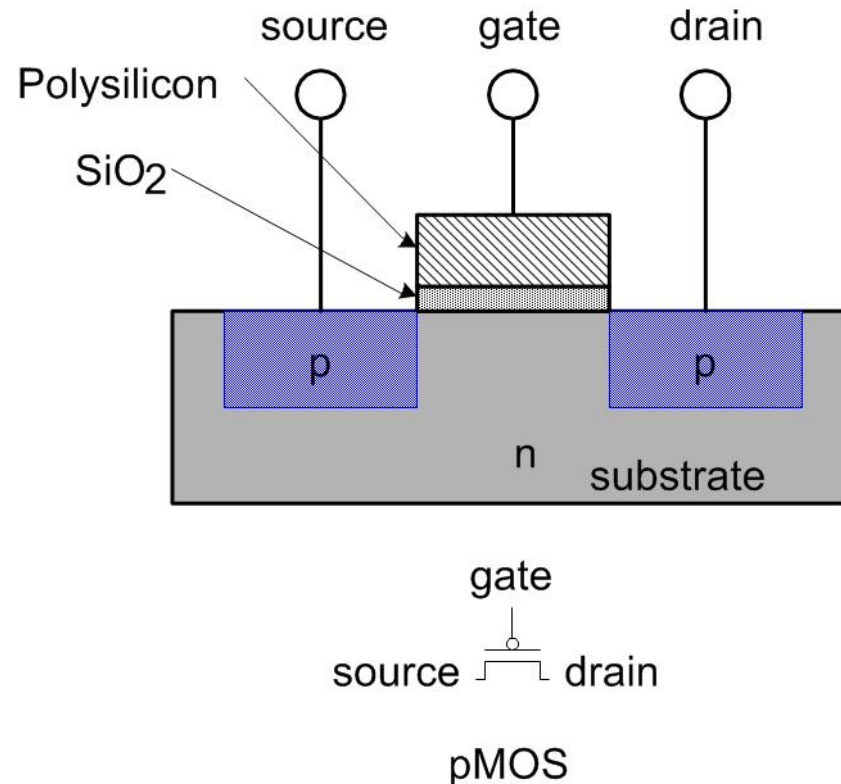
## pMOS transistor is opposite

- **ON** when **Gate = 0**
- **OFF** when **Gate = 1**




# Transistor Function


nMOS

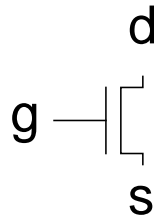




$g = 0$

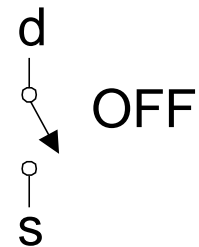

$g = 1$

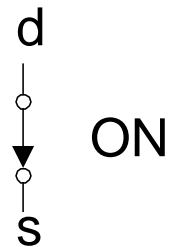

pMOS

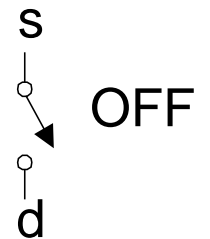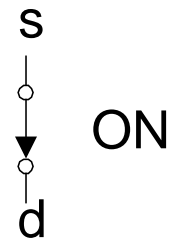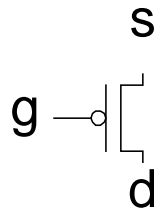


# Chapter 1: From Zero to One

## **Gates from Transistors**

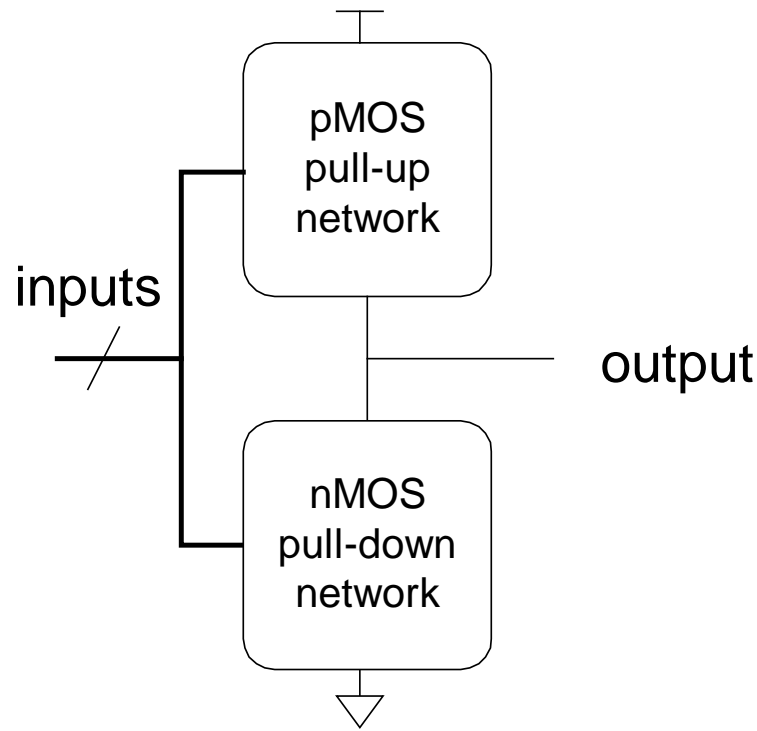
# Transistor Function

- **nMOS**: pass good **0**'s, so connect source to GND
- **pMOS**: pass good **1**'s, so connect source to  $V_{DD}$




# CMOS Gates: NOT Gate

**NOT**

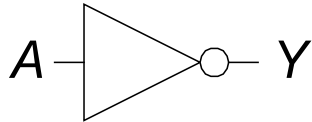

$$Y = \overline{A}$$


A	Y
0	1
1	0

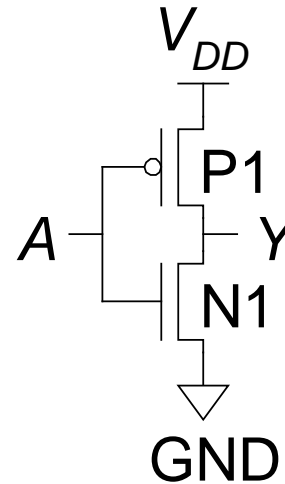

A	P1	N1	Y
0			
1			


# CMOS Gates: NAND Gate

## NAND

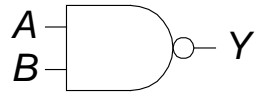


$$Y = \overline{AB}$$

A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

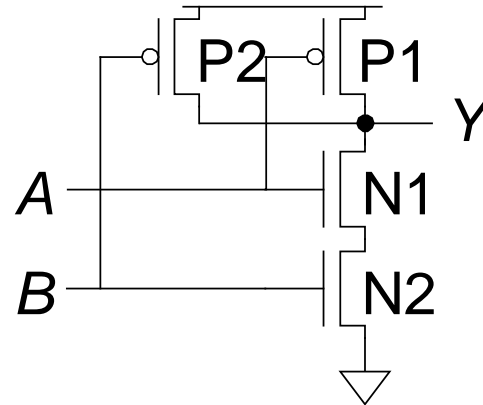

A	B	P1	P2	N1	N2	Y
0	0					
0	1					
1	0					
1	1					


# CMOS Gate Structure

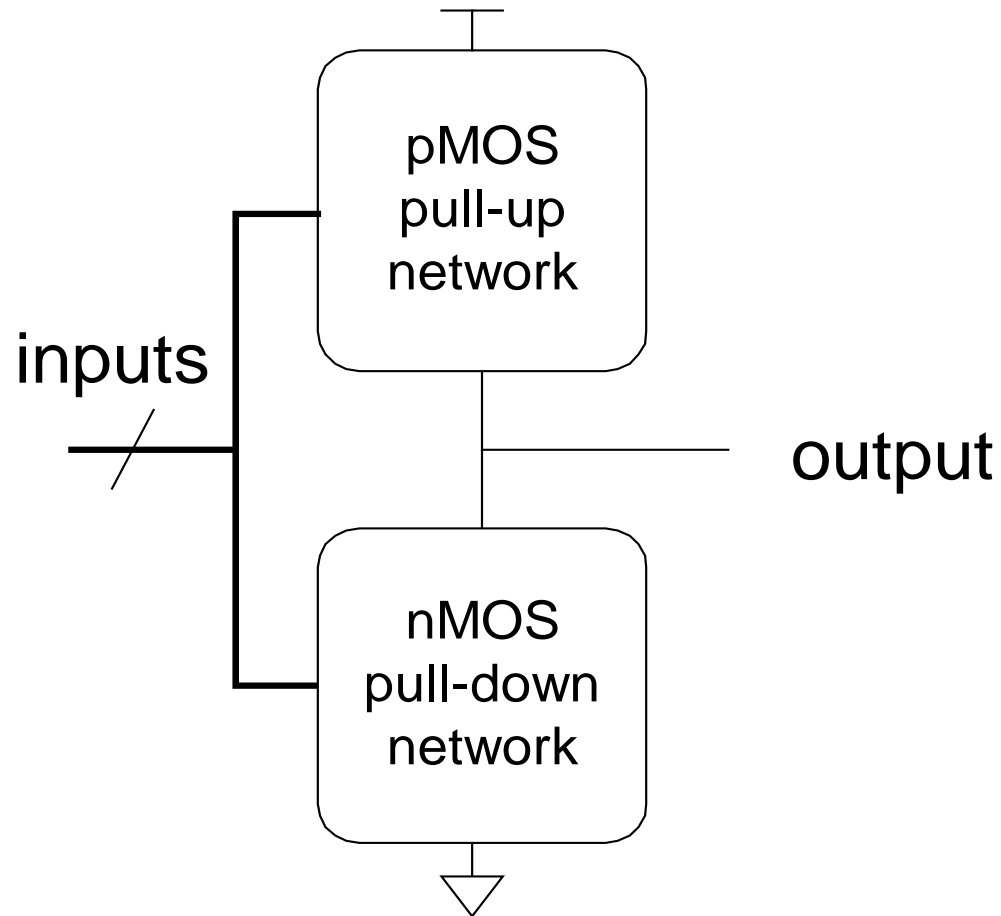




# NOR3 Gate

How do you build a three-input NOR gate?

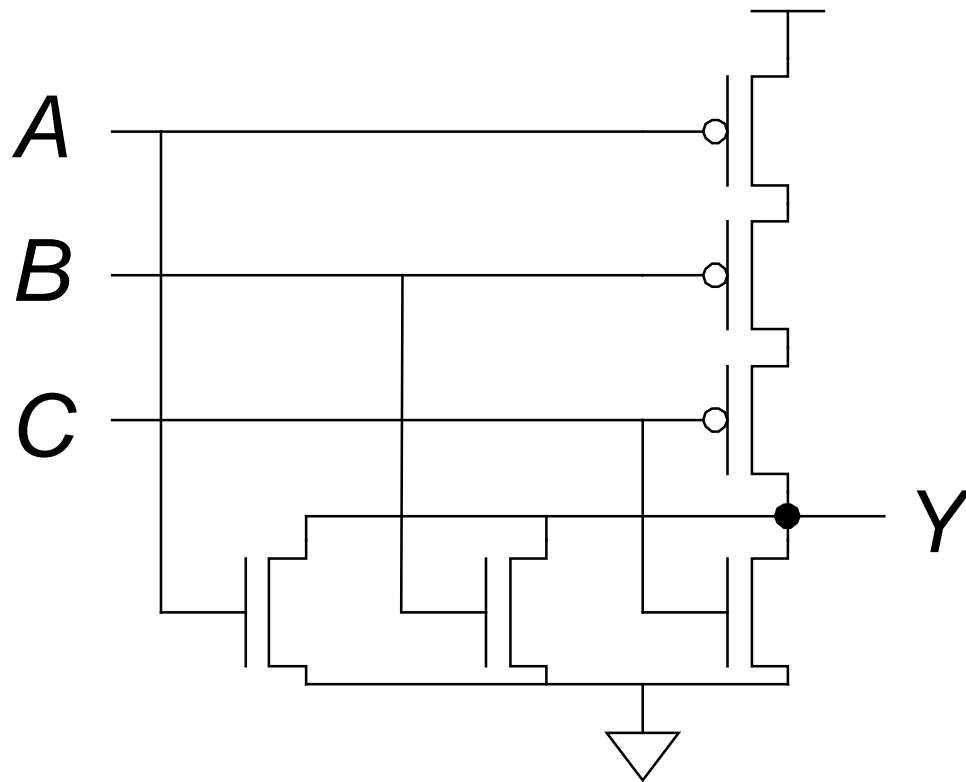


# AND2 Gate

How do you build a two-input AND gate?

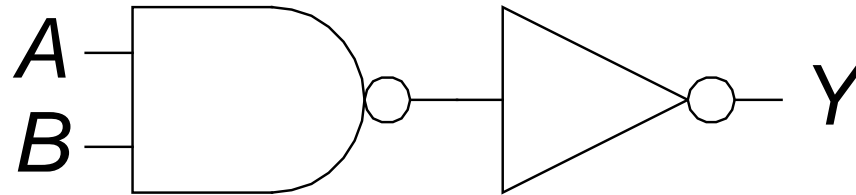

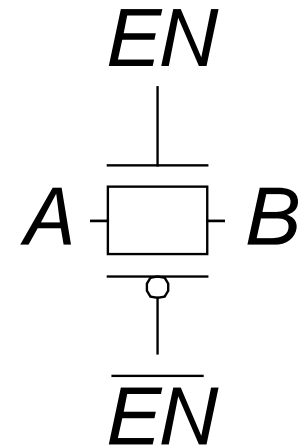
# Transmission Gates

- nMOS pass 1's poorly
- pMOS pass 0's poorly
- The parallel combination of the two passes, or a *transmission gate* is a better switch
  - passes both 0 and 1 well
- When  $EN = 1$ , the switch is ON:
  - $\overline{EN} = 0$  and  $A$  is connected to  $B$
- When  $EN = 0$ , the switch is OFF:
  - $A$  is not connected to  $B$



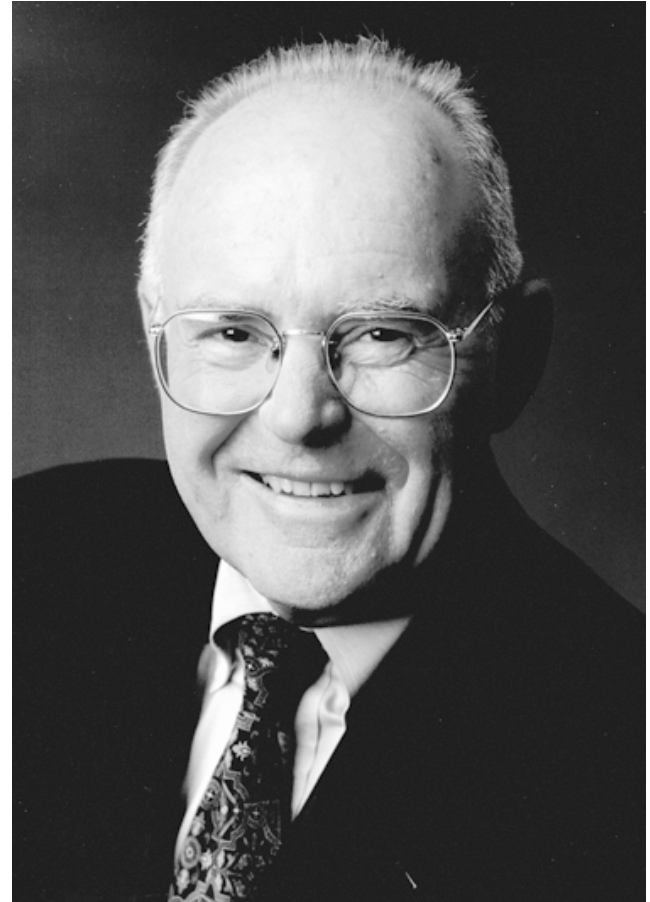
# Gordon Moore, 1929-

- Cofounded Intel in 1968 with Robert Noyce.
- **Moore's Law:** number of transistors on a computer chip doubles every year (observed in 1965)
- Since 1975, transistor counts have doubled every two years.
- Corollaries: transistors get faster and lower power



# Moore's Law

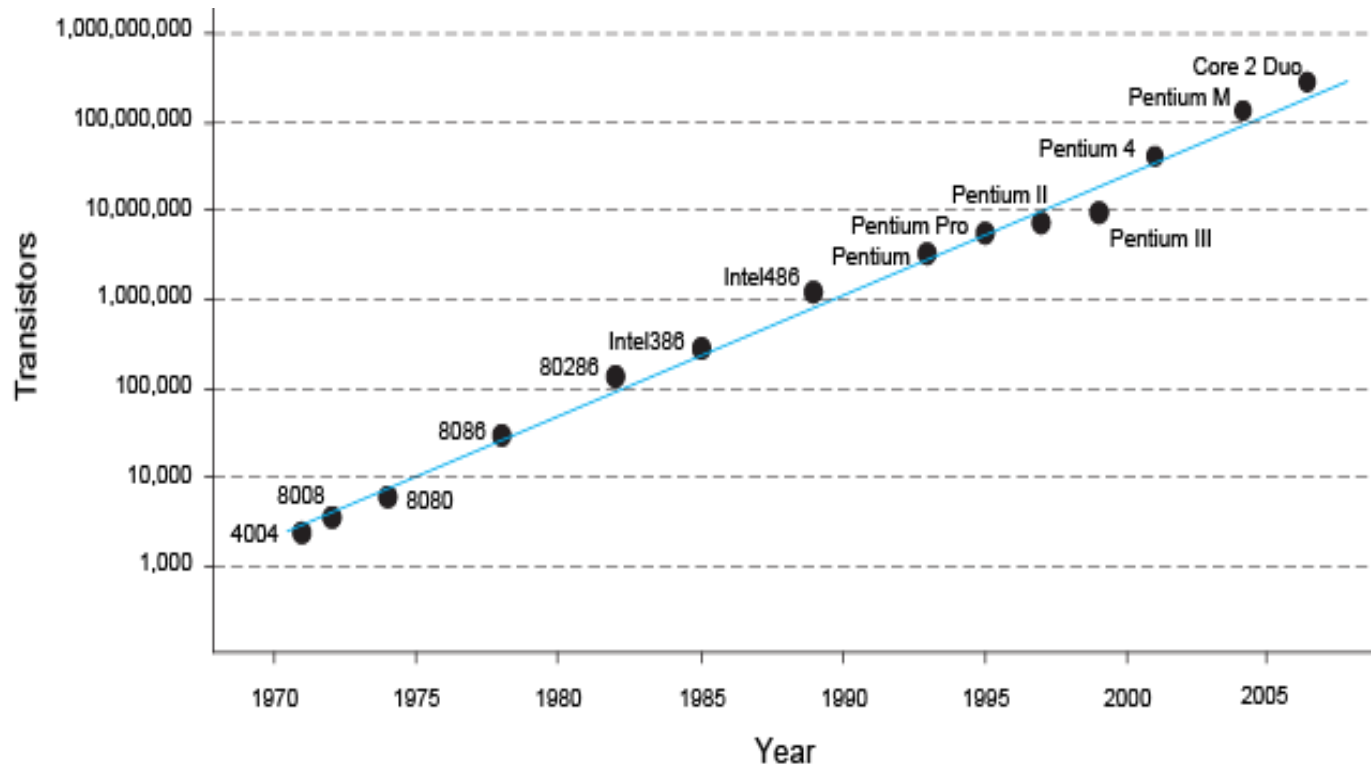

*“If the automobile had followed the same development cycle as the computer, a Rolls-Royce would today cost \$100, get one million miles to the gallon, and explode once a year . . .” (Robert Cringely, Infoworld)*

*– Robert Cringely*

## Chapter 1: From Zero to One

# Power Consumption

# Power Consumption

**Power = Energy consumed per unit time**

- Dynamic power consumption
- Static power consumption

# Dynamic Power Consumption

- **Power to charge transistor gate capacitances**
  - Energy required to charge a capacitance,  $C$ , to  $V_{DD}$  is  $CV_{DD}^2$
  - Circuit running at frequency  $f$  ( $f$  cycles per second)
  - Capacitor is charged  $\alpha$  times per cycle (discharging from 1 to 0 is free)
- **Dynamic power consumption:**

$$P_{dynamic} = \alpha CV_{DD}^2 f$$



# Static Power Consumption

- Power consumed when no gates are switching
- Caused by the *quiescent supply current*,  $I_{DD}$  (also called the *leakage current*)
- Static power consumption:

$$P_{static} = I_{DD}V_{DD}$$

# Power Consumption Example

- Estimate the power consumption of a mobile phone running Angry Birds
  - $V_{DD} = 0.8 \text{ V}$
  - $C = 5 \text{ nF}$  ( $5 \times 10^{-9} \text{ Farads}$ )
  - $f = 2 \text{ GHz}$  ( $2 \times 10^9 \text{ Hertz}$ )
  - $\alpha = 0.1$
  - $I_{DD} = 100 \text{ mA}$

$$\begin{aligned} P &= \alpha C V_{DD}^2 f + I_{DD} V_{DD} \\ &= (0.1)(5 \text{ nF})(0.8 \text{ V})^2(2 \text{ GHz}) + (100 \text{ mA})(0.8 \text{ V}) \\ &= (0.64 + 0.08) \text{ W} \approx 0.72 \text{ W} \end{aligned}$$

# Power Consumption Example

- If the phone has a 8 W-hr battery, estimate its battery life sitting idle in your pocket.
  - $V_{DD} = 0.8 \text{ V}$
  - $I_{DD} = 100 \text{ mA}$

$$P_{static} = I_{DD} V_{DD} = 0.08 \text{ W}$$

$$\begin{aligned} \text{Battery life} &= \text{Capacity} / \text{Consumption} \\ &= (8 \text{ W-hr}) / (0.08 \text{ W}) = 100 \text{ hr (4 days)} \end{aligned}$$