

# Digital Design & Computer Architecture










Sarah Harris & David Harris

## Chapter 3: Sequential Logic Design

*Modified by Younghwan Yoo, 2023*
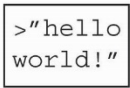
# Chapter 3 :: Topics

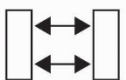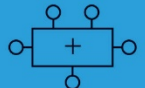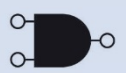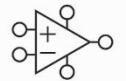- **State Elements**
  - Bistable Circuit
  - SR Latch
  - D Latch
  - D Flip-Flop
  - Variations
- **Synchronous Sequential Logic**
- **Finite State Machines**
  - Moore
  - Mealy
- **Metastability**
- **Parallelism**

Application Software	
Operating Systems	
Architecture	
Micro-architecture	
Logic	
Digital Circuits	
Analog Circuits	
Devices	
Physics	

# Chapter 3: Sequential Logic

## **State Elements**

# Introduction

- Outputs of sequential logic depend on current *and* prior input values – it has ***memory***.
- Some definitions:
  - **State:** all the information about a circuit necessary to explain its future behavior
  - **Latches and flip-flops:** state elements that store one bit of state
  - **Synchronous sequential circuits:** sequential circuits using flip-flops sharing a common clock

# Sequential Circuits

- Give sequence to events
- Have memory (short-term)
- Use feedback from output to input to store information

# State Elements

- **State:** everything about the prior inputs to the circuit necessary to predict its future behavior
  - Usually just 1 bit, the last value captured
- State elements store state
  - Bistable circuit
  - SR Latch
  - D Latch
  - D Flip-flop


# Chapter 3: Sequential Logic

## **Bistable Circuit**


# Bistable Circuit

- Fundamental building block of other state elements
- Two outputs:  $Q$ ,  $\overline{Q}$
- No inputs

Same circuit!

 

Back-to-back inverters

 

Cross-coupled inverters



# Bistable Circuit Analysis


- Consider the two possible cases:

–  $Q = 0$ :

then  $\bar{Q} = 1$ ,  $Q = 0$  (consistent)

–  $Q = 1$ :

 then  $\bar{Q} = 0$ ,  $Q = 1$  (consistent)




- Stores 1 bit of state in the state variable, Q (or  $\bar{Q}$ )
- But there are **no inputs to control the state**

# Chapter 3: Sequential Logic

## **SR Latch**

# SR (Set/Reset) Latch

- **SR Latch**

 


- Consider the four possible cases:
  - **$S = 1, R = 0$**
  - **$S = 0, R = 1$**
  - **$S = 0, R = 0$**
  - **$S = 1, R = 1$**

# SR Latch Analysis

–  $S = 1, R = 0$ :

then  $Q = 1$  and  $\bar{Q} = 0$


**Set the output**

 

–  $S = 0, R = 1$ :

then  $Q = 0$  and  $\bar{Q} = 1$

**Reset the output**

 


# SR Latch Analysis

–  $S = 0, R = 0$ :


then  $Q = Q_{prev}$

**Memory!**

$Q_{prev} = 0$

 

$Q_{prev} = 1$

 


–  $S = 1, R = 1$ :

then  $Q = 0, \overline{Q} = 0$

**Invalid State**


$\overline{Q} \neq \text{NOT } Q$

 

# SR Latch

- **SR** stands for **S**et/**R**eset latch
  - Stores one bit of state ( $Q$ )
- Control what value is being stored with  $S$ ,  $R$  inputs
  - **Set**: make the output 1  
 $S = 1, R = 0, Q = 1$
  - **Reset**: make the output 0  
 $S = 0, R = 1, Q = 0$
  - **Memory**: retain value  
 $S = 0, R = 0, Q = Q_{prev}$

SR Latch  
Symbol

 

- **Must do something to avoid invalid state (when  $S = R = 1$ )**


# Chapter 3: Sequential Logic

## **D Latch**

# D Latch


- **Two inputs:  $CLK$ ,  $D$** 
  - $CLK$ : controls *when* the output changes
  - $D$  (the data input): controls *what* the output changes to
- **Function**
  - When  $CLK = 1$ ,  
 $D$  passes through to  $Q$  (*transparent*)
  - When  $CLK = 0$ ,  
 $Q$  holds its previous value (*opaque*)
- **Avoids invalid case where**  
$$Q \neq \text{NOT } \bar{Q}$$

D Latch  
Symbol

 



# D Latch Internal Circuit

 

$CLK$	$D$	$\overline{D}$	$S$	$R$	$Q$	$\overline{Q}$
0	X	$\overline{X}$	0	0	$Q_{prev}$	$\overline{Q}_{prev}$
1	0	1	0	1	0	1
1	1	0	1	0	1	0



# Chapter 3: Sequential Logic

## **D Flip-Flop**


# D Flip-Flop


- **Inputs:**  $CLK$ ,  $D$
- **Function:**
  - **Samples  $D$  on rising edge of  $CLK$** 
    - When  $CLK$  rises from 0 to 1,  $D$  passes through to  $Q$
    - Otherwise,  $Q$  holds its previous value
  - **$Q$  changes** only on rising edge of  $CLK$
- Called **edge-triggered**
  - Activated on the *clock edge*

D Flip-Flop Symbols

  


## D Flip-Flop Internal Circuit

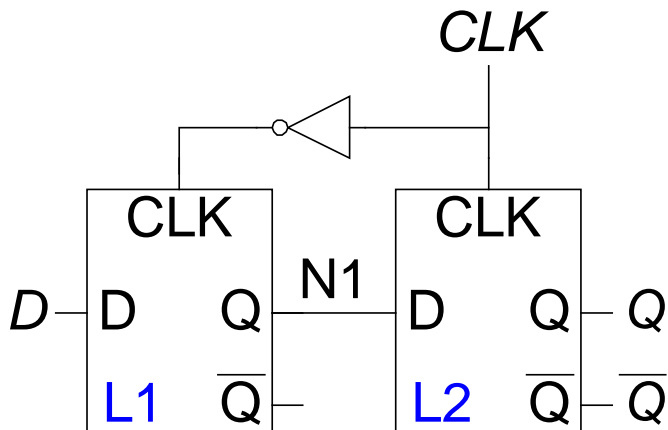- **Two back-to-back D latches (L1 and L2)** controlled by complementary clocks
  - When  **$CLK = 0$** 
    - L1 is transparent
    - L2 is opaque
    - **$D$**  passes through to  **$N1$**
  - When  **$CLK = 1$** 
    - L2 is transparent
    - L1 is opaque
    - **$N1$**  passes through to  **$Q$**
  - Thus, on the edge of the clock (when  **$CLK$  rises from 0  $\rightarrow$  1**)
    - **$D$**  passes through to  **$Q$**
- 
- ```
graph LR
    D((D)) --> L1[D L1]
    L1_Q[Q] -- N1 --> L2_D[D L2]
    L1_Q --> Q_bar1[Q-bar]
    CLK --> L1_CLK[CLK]
    CLK --> Inv[Inverter]
    Inv --> L2_CLK[CLK]
    L2_Q[Q] --> Q[Q]
    L2_Q --> Q_bar2[Q-bar]
```

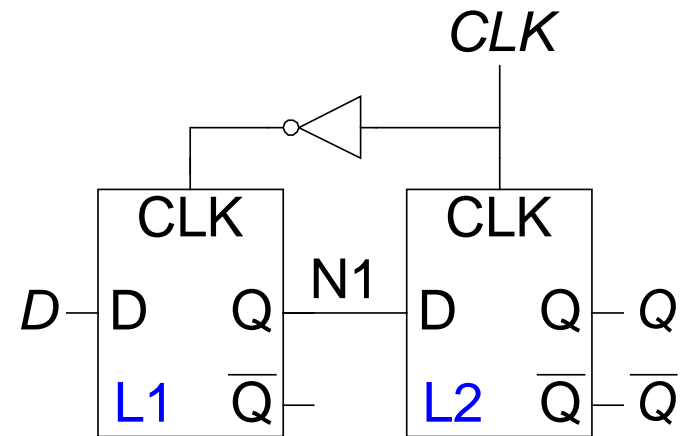

 
# D Latch vs. D Flip-Flop

Level-sensitive,  
transparent  
when CLK=1




 **D Latch**

Edge-triggered,  
copies D to Q on  
the rising edge




**D Flip-flop**

 


## Chapter 3: Sequential Logic

# Variations on a Flop

# Registers: One or More Flip-flops

 

**4-bit Register**

 


Two ways to draw a register



# Enabled Flip-Flops

- **Inputs:**  $CLK$ ,  $D$ ,  $EN$ 
  - The enable input ( $EN$ ) controls when new data ( $D$ ) is stored
- **Function**
  - $EN = 1$ :  $D$  passes through to  $Q$  on the clock edge
  - $EN = 0$ : the flip-flop retains its previous state

Symbol

 

Internal circuits

  




# Resettable Flip-Flops


- **Inputs:** *CLK*, *D*, *Reset*
- **Function:**
  - **Reset = 1:** *Q* is forced to 0
  - **Reset = 0:** flip-flop behaves as ordinary D flip-flop

## Symbols

 
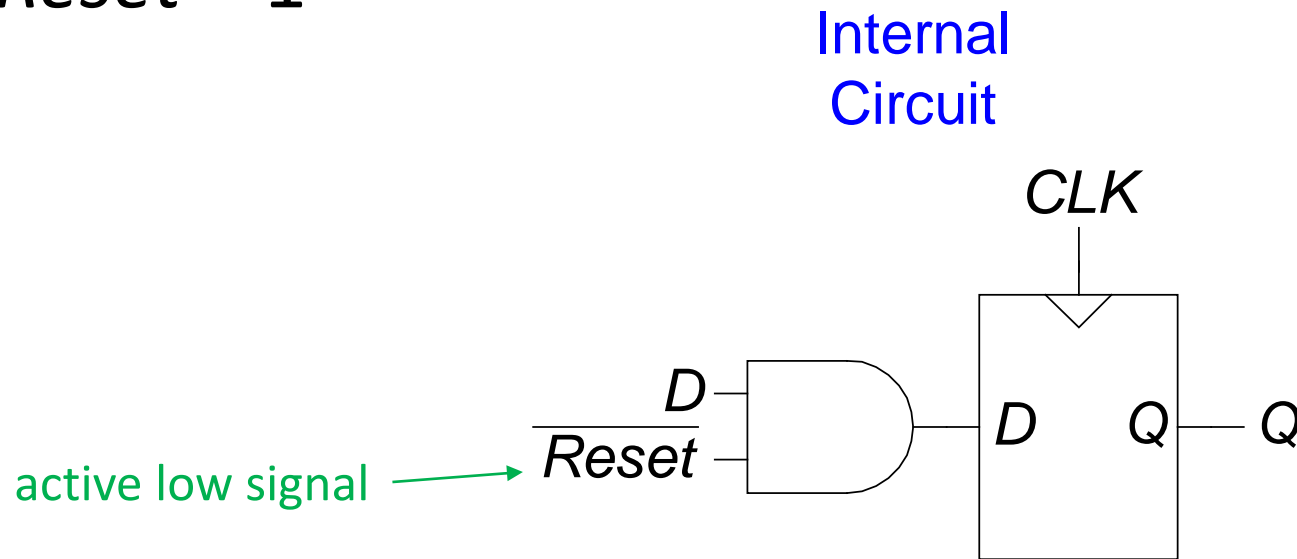
# Resettable Flip-Flops


- Two types:
  - **Synchronous:** resets at the clock edge only
  - **Asynchronous:** resets immediately when  $Reset = 1$



# Settable Flip-Flops

- **Inputs:**  $CLK$ ,  $D$ ,  $Set$
- **Function:**
  - **$Set = 1$ :**  $Q$  is set to 1
  - **$Set = 0$ :** the flip-flop behaves as ordinary D flip-flop

## Symbols


 


## Chapter 3: Sequential Logic

# **Synchronous Sequential Logic**
  
# Sequential Logic

- **Sequential circuits:** include all circuits that aren't combinational
- **A problematic circuit:**




- **No inputs** and 1-3 outputs
- *Astable* (or *unstable*) circuit, **oscillates**
- Period depends on inverter delay (1 ns)
- It has a **cyclic path**: output fed back to input

# Race Condition

- An improved (?) D latch


| $CLK$ | $D$ | $Q_{prev}$ | $Q$ |
|-------|-----|------------|-----|
| 0     | 0   | 0          | 0   |
| 0     | 0   | 1          | 1   |
| 0     | 1   | 0          | 0   |
| 0     | 1   | 1          | 1   |
| 1     | 0   | 0          | 0   |
| 1     | 0   | 1          | 0   |
| 1     | 1   | 0          | 1   |
| 1     | 1   | 1          | 1   |
 
$$Q = CLK \cdot D + \overline{CLK} \cdot Q_{prev}$$



- Suppose  $D=CLK=1$ , then  $Q=1$
- $CLK \rightarrow 0$ , then  $N1 \rightarrow 0$ ,  $N2 \rightarrow 1$  expected
- If the delay of the NOT gate is long,  $Q \rightarrow 0$  while  $\overline{CLK}$  is still 0, then  $Q_{prev} \rightarrow 0$  and  $Q$  stuck at 0 forever

**Race  
condition**

 

# Synchronous Sequential Logic Design

- Cyclic paths can have unstable behavior
- Breaks cyclic paths by **inserting registers**, transforming the circuit into a collection of combinational logic and registers
  - Registers contain state of the system
  - State changes only at clock edge: system synchronized to the clock
- **Rules** of synchronous sequential circuit composition:
  - Every circuit element is either a **register** or a **combinational circuit**
  - At least **one** circuit element is a **register**
  - All registers receive the **same clock**
  - Every **cyclic path** contains at least **one register**
- Two common synchronous sequential circuits
  - **Finite State Machines (FSMs)**
  - **Pipelines**

# Chapter 3: Sequential Logic

**FSMs:**

**Finite State Machines**




# Finite State Machine (FSM)

- **Consists of:**



- **State register**

 - Stores current state
    - Loads next state at clock edge



- **Combinational logic**

  - Computes the next state
    - Computes the outputs




# Finite State Machines (FSMs)


- **Next state** determined by **current state** and **inputs**
- Two types of finite state machines differ in **output** logic:
  - **Moore FSM:** outputs depend **only** on **current state**
  - **Mealy FSM:** outputs depend on **current state** *and* **inputs**

# Finite State Machines (FSMs)

## Moore FSM

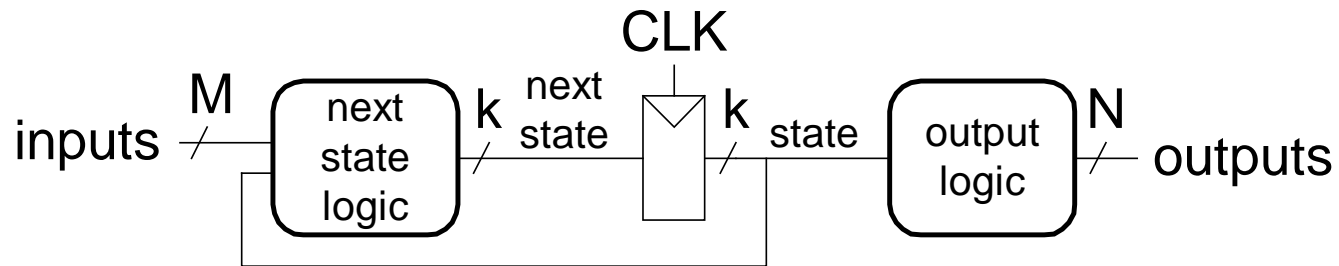

## Mealy FSM

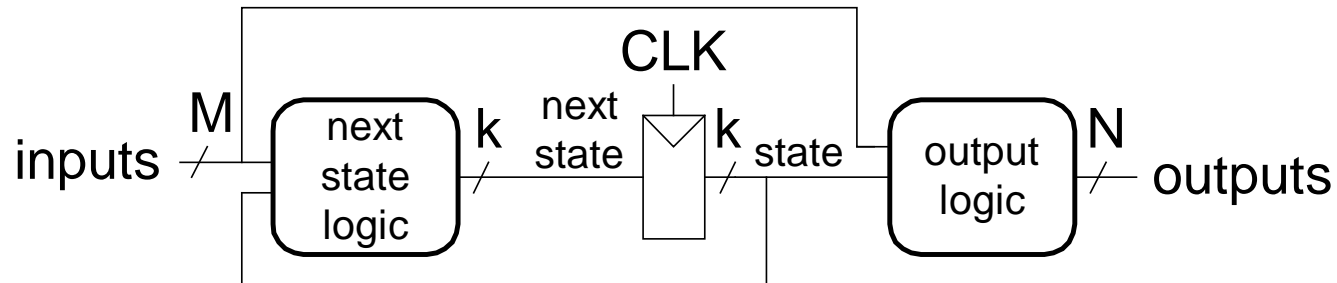

# FSM Design Procedure


1. Identify **inputs** and **outputs**
2. Sketch **state transition diagram**
3. Write **state transition table** and **output table**
  - **Moore FSM:** write **separate** tables
  - **Mealy FSM:** write **combined** state transition and output table
4. Select **state encodings** represented in binary forms
5. Rewrite state transition table and output table with state **encodings**
6. Write **Boolean equations** for next state and output logic
7. Sketch the circuit **schematic**

## Chapter 3: Sequential Logic

# Moore FSM Example

 
# FSM Example

- **Traffic light controller**
  - Traffic sensors:  $T_A$ ,  $T_B$  (TRUE when there's traffic)
  - Lights:  $L_A$ ,  $L_B$



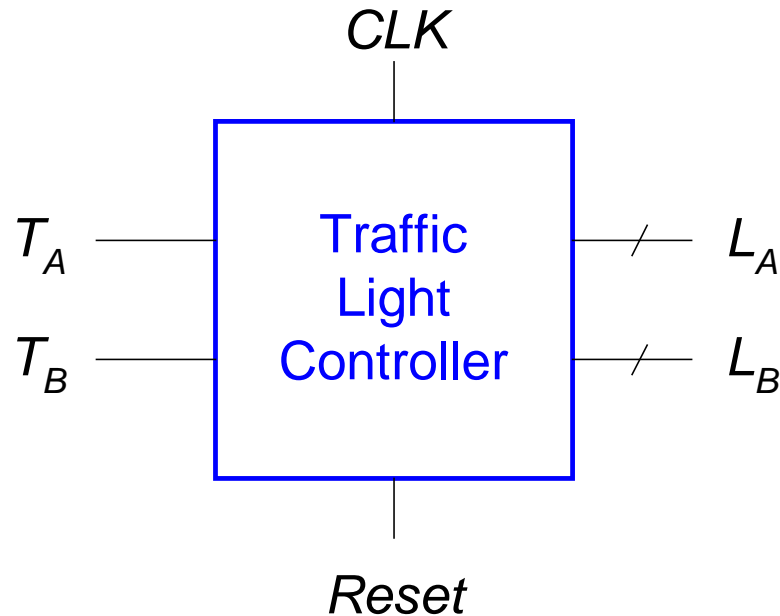
# FSM Black Box

- **Inputs:**  $CLK$ ,  $Reset$ ,  $T_A$ ,  $T_B$
- **Outputs:**  $L_A$ ,  $L_B$


 
# FSM State Transition Diagram


- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs




 
# FSM State Transition Diagram

- **Moore FSM:** outputs labeled in each state
- **States:** Circles
- **Transitions:** Arcs




# FSM State Transition Table

| Current State<br>$S$ | Inputs |       | Next State<br>$S'$ |
|----------------------|--------|-------|--------------------|
|                      | $T_A$  | $T_B$ |                    |
| S0                   | 0      | X     |                    |
| S0                   | 1      | X     |                    |
| S1                   | X      | X     |                    |
| S2                   | X      | 0     |                    |
| S2                   | X      | 1     |                    |
| S3                   | X      | X     |                    |

$S$ : Current State

$S'$ : Next State

 

# FSM Encoded State Transition Table

| Current State |       | Inputs |       | Next State |        |
|---------------|-------|--------|-------|------------|--------|
| $s_1$         | $s_0$ | $T_A$  | $T_B$ | $s'_1$     | $s'_0$ |
| 0             | 0     | 0      | X     | 0          | 1      |
| 0             | 0     | 1      | X     | 0          | 0      |
| 0             | 1     | X      | X     | 1          | 0      |
| 1             | 0     | X      | 0     | 1          | 1      |
| 1             | 0     | X      | 1     | 1          | 0      |
| 1             | 1     | X      | X     | 0          | 0      |


$$s'_1 = \overline{s_1}s_0 + s_1\overline{s_0}\overline{T_B} + s_1\overline{s_0}T_B = \overline{s_1}s_0 + s_1\overline{s_0} = s_1 \oplus s_0$$

$$s'_0 = \overline{s_1}\overline{s_0}T_A + s_1\overline{s_0}\overline{T_B}$$

| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |
| S3    | 11       |

# FSM Output Table

| Current State |       | Outputs  |          |          |          |
|---------------|-------|----------|----------|----------|----------|
| $S_1$         | $S_0$ | $L_{A1}$ | $L_{A0}$ | $L_{B1}$ | $L_{B0}$ |
|               | S0    | green    |          | red      |          |
|               | S1    | yellow   |          | red      |          |
|               | S2    | red      |          | green    |          |
|               | S3    | red      |          | yellow   |          |

 

$$L_{A1} = S_1 \bar{S}_0 + \bar{S}_1 S_0 = S_1$$


$$L_{A0} = \bar{S}_1 S_0$$

$$L_{B1} = \bar{S}_1 \bar{S}_0 + S_1 S_0 = \bar{S}_1$$

$$L_{B0} = S_1 S_0$$

| Output | Encoding |
|--------|----------|
| green  | 00       |
| yellow | 01       |
| red    | 10       |

# FSM Schematic

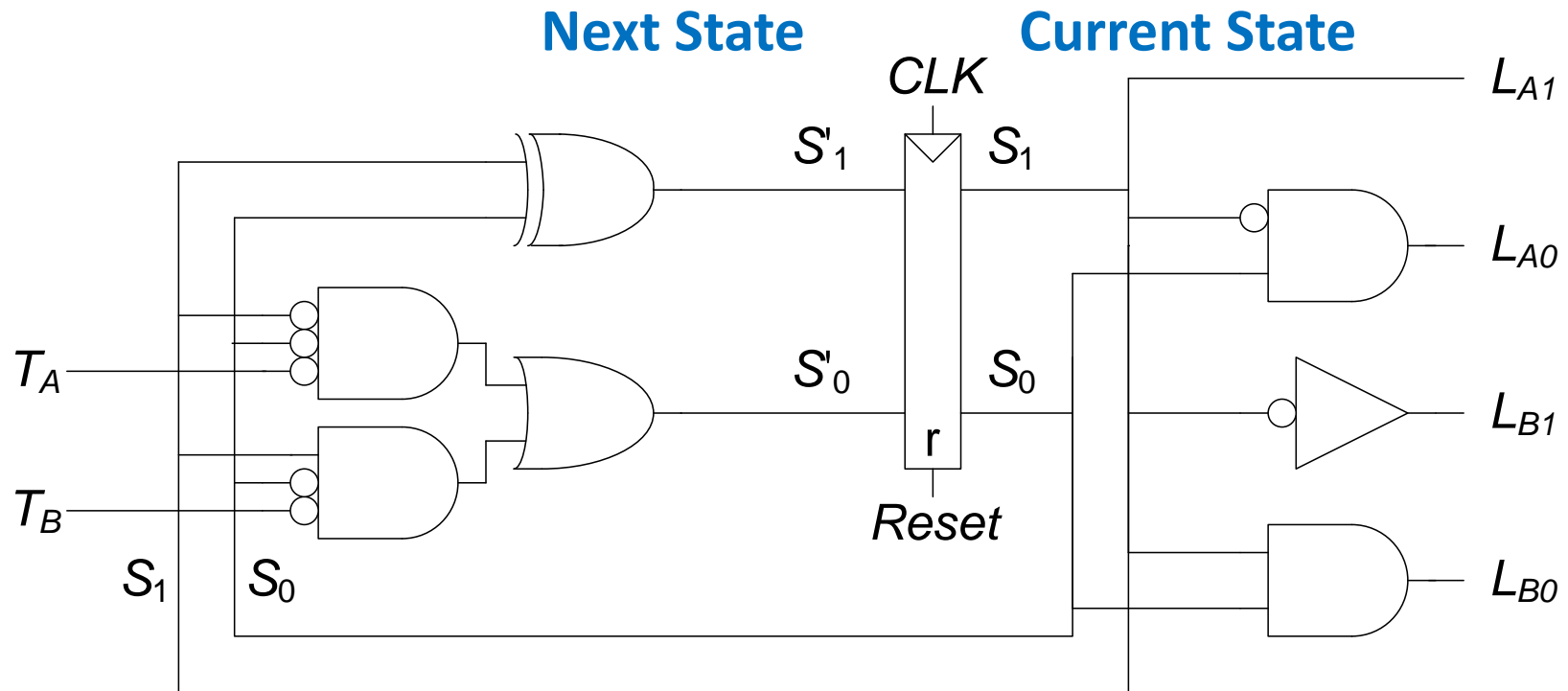

## Next State Logic

$$S'_1 = S_1 \oplus S_0$$

$$S'_0 = \overline{S_1} \overline{S_0} \overline{T_A} + S_1 \overline{S_0} \overline{T_B}$$

## State Register

## Output Logic



$$L_{A1} = S_1$$

$$L_{A0} = \overline{S_1} S_0$$

$$L_{B1} = \overline{S_1}$$

$$L_{B0} = S_1 S_0$$

# FSM Timing Diagram

  

# State Encodings

- **Binary** encoding
  - i.e., for four states, 00, 01, 10, 11
- **One-hot** encoding
  - One state bit per state
  - Only one state bit HIGH at once
  - i.e., for 4 states, 0001, 0010, 0100, 1000
  - Requires more flip-flops
  - Often next state and output logic is simpler

# 1-Hot State Encoding Example


| Current State |       |       |       | Inputs |       | Next State |        |        |        |
|---------------|-------|-------|-------|--------|-------|------------|--------|--------|--------|
| $s_3$         | $s_2$ | $s_1$ | $s_0$ | $T_A$  | $T_B$ | $s'_3$     | $s'_2$ | $s'_1$ | $s'_0$ |
|               | S0    |       |       | 0      | X     |            | S1     |        |        |
|               | S0    |       |       | 1      | X     |            | S0     |        |        |
|               | S1    |       |       | X      | X     |            | S2     |        |        |
|               | S2    |       |       | X      | 0     |            | S3     |        |        |
|               | S2    |       |       | X      | 1     |            | S2     |        |        |
|               | S3    |       |       | X      | X     |            | S0     |        |        |

$$s'_3 = s_2 \overline{T_B}$$

$$s'_2 = s_1 + s_2 T_B$$

$$s'_1 = s_0 \overline{T_A}$$

$$s'_0 = s_0 T_A + s_3$$

 

| State | 1-Hot Encoding |
|-------|----------------|
| S0    | 0001           |
| S1    | 0010           |
| S2    | 0100           |
| S3    | 1000           |




## Chapter 3: Sequential Logic

# **Mealy FSM Example**
 
# Moore vs. Mealy FSMs


Alyssa P. Hacker has a snail that crawls down a paper tape with 1's and 0's on it. The snail smiles whenever the last two digits it has crawled over are **01**. Design **Moore** and **Mealy** FSMs to compute when the snail should smile.

- **Moore FSM**: outputs depend **only** on current state
- **Mealy FSM**: outputs depend on current state *and* inputs




# State Transition Diagrams

## Moore FSM

 

## Mealy FSM

 


Output:  
"The snail smiles."

# Moore FSM State Transition Table

| Current State |       | Inputs | Next State |        |
|---------------|-------|--------|------------|--------|
| $s_1$         | $s_0$ |        | $s'_1$     | $s'_0$ |
| 0             | 0     | 0      | 0          | 1      |
| 0             | 0     | 1      | 0          | 0      |
| 0             | 1     | 0      | 0          | 1      |
| 0             | 1     | 1      | 1          | 0      |
| 1             | 0     | 0      | 0          | 1      |
| 1             | 0     | 1      | 0          | 0      |

| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |

 


$$s'_1 = \overline{s_0}A$$

$$s'_0 = A$$

# Moore FSM Output Table

| Current State |       | Output |
|---------------|-------|--------|
| $s_1$         | $s_0$ | $Y$    |
| 0             | 0     |        |
| 0             | 1     |        |
| 1             | 0     |        |


| State | Encoding |
|-------|----------|
| S0    | 00       |
| S1    | 01       |
| S2    | 10       |

 

# Mealy State Transition & Output Table

| Current State | Input | Next State | Output |
|---------------|-------|------------|--------|
| $S_0$         | $A$   | $S'_0$     | $Y$    |
| 0             | 0     |            |        |
| 0             | 1     |            |        |
| 1             | 0     |            |        |
| 1             | 1     |            |        |

| State | Encoding |
|-------|----------|
| S0    | 0        |
| S1    | 1        |

 

# Moore FSM Schematic


## Next State Equations

$$S_1' = S_0 A$$

$$S_0' = \overline{A}$$

## Output Equation

$$Y = S_1$$

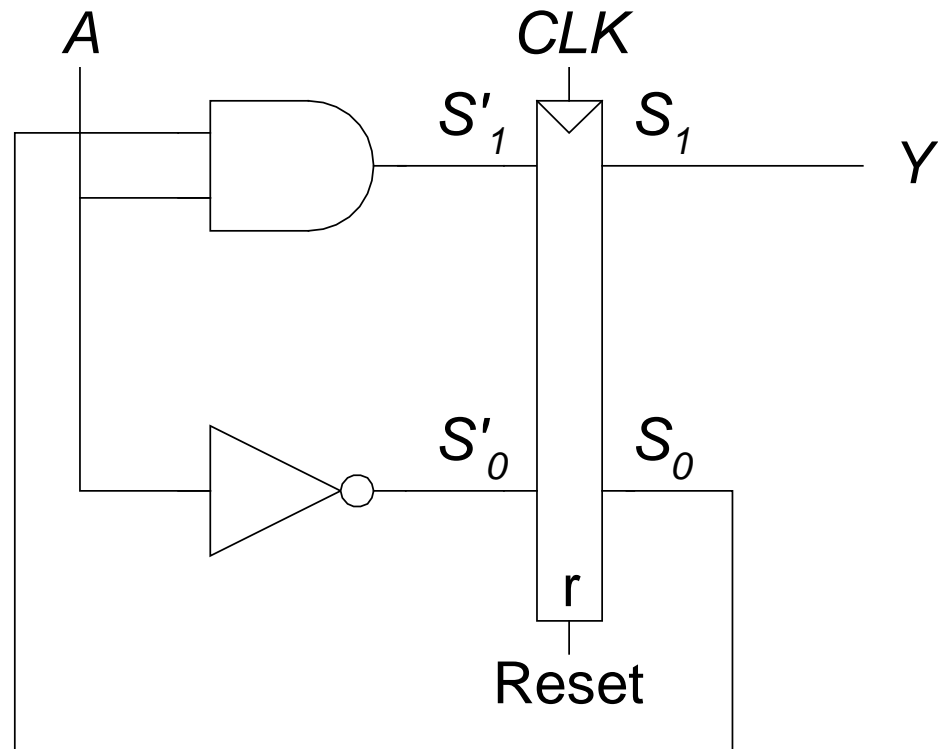


# Mealy FSM Schematic

## Next State Equation

$$S_0' = \overline{A}$$


## Output Equation

$$Y = S_0 A$$

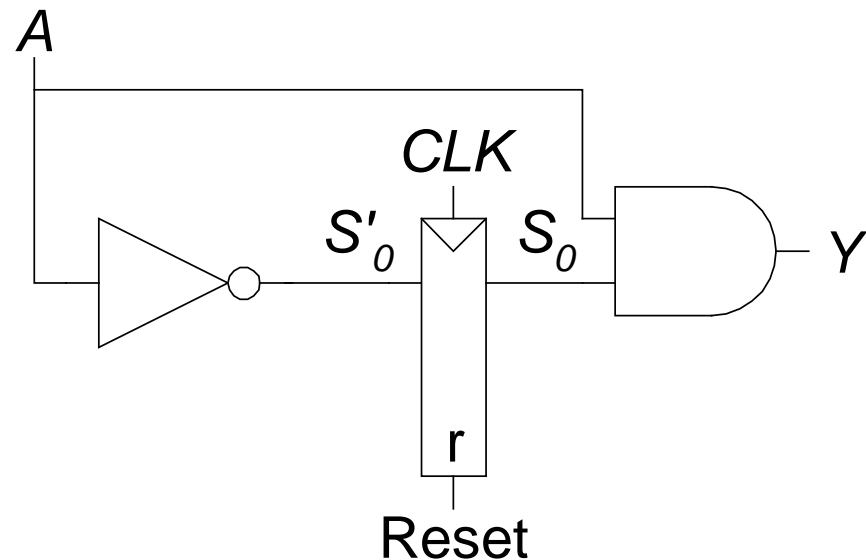





# Moore and Mealy Timing Diagram

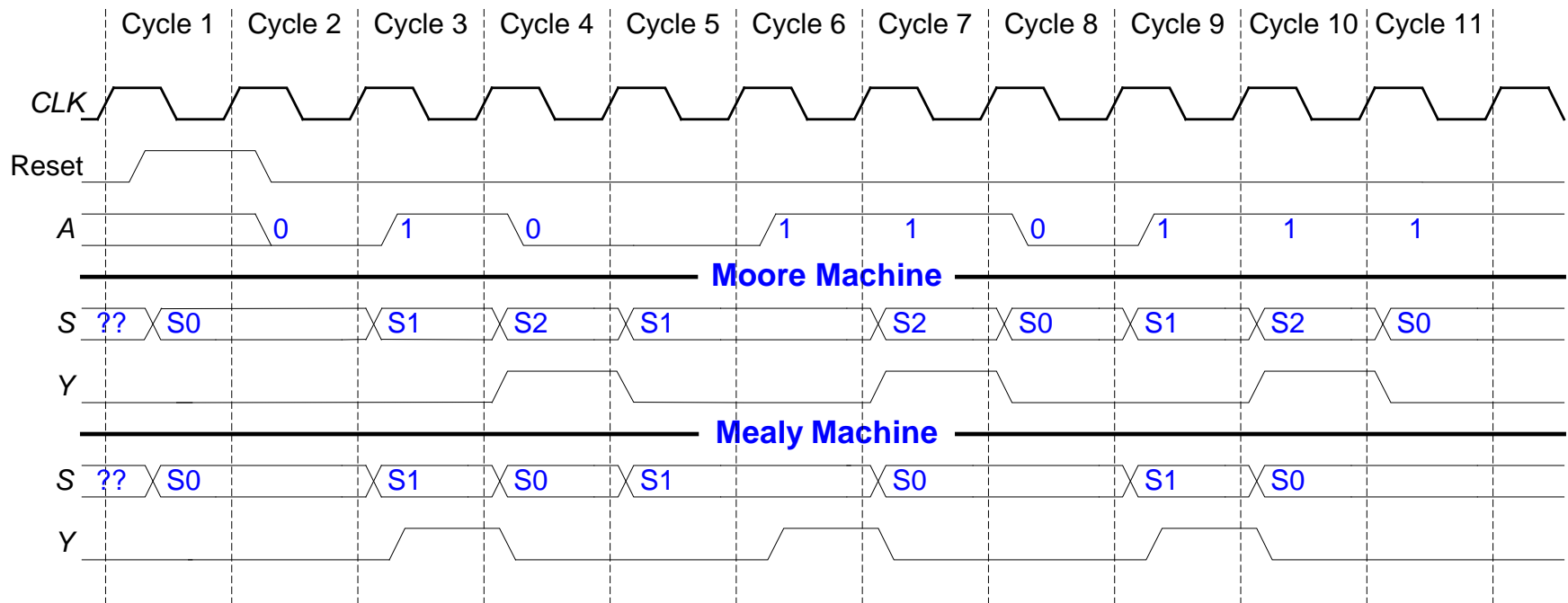

Moore FSM

 

Mealy FSM

 

**Mealy FSM:** asserts Y **immediately** when input pattern 01 is detected

**Moore FSM:** asserts Y one cycle **after** input pattern 01 is detected

# Chapter 3: Sequential Logic

## **Timing**



# Timing

- Flip-flop samples  $D$  at clock edge
- **$D$  must be stable when sampled**
- Similar to a photograph,  $D$  must be stable around clock edge
  - If an object moves while taking a picture, the image will be blurred.



 
 
# Input Timing Constraints

- **Setup time:**  $t_{\text{setup}}$  = time *before* clock edge data must be stable (i.e. not changing)
- **Hold time:**  $t_{\text{hold}}$  = time *after* clock edge data must be stable
- **Aperture time:**  $t_a$  = time *around* clock edge data must be stable ( $t_a = t_{\text{setup}} + t_{\text{hold}}$ )


  
# Output Timing Constraints

- **Clock-to-Q propagation delay,  $t_{pcq}$** : time after clock edge that  $Q$  is guaranteed to be stable (i.e., to stop changing): **maximum delay** (*clock-to-Q propagation delay*)
- **Clock-to-Q contamination delay,  $t_{ccq}$** : time after clock edge that  $Q$  might be unstable (i.e., start changing): **minimum delay**




# Dynamic Discipline

- Synchronous sequential circuit inputs must be **stable during aperture** (setup and hold) time around clock edge
- Specifically, inputs must be stable
  - at least  $t_{\text{setup}}$  before the clock edge
  - at least until  $t_{\text{hold}}$  after the clock edge

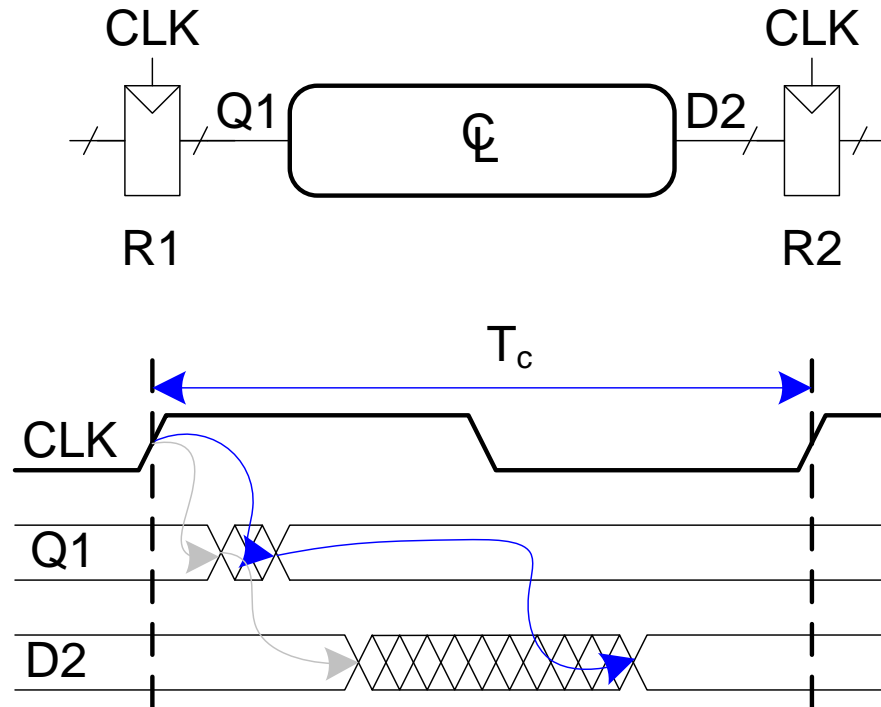
# Dynamic Discipline

- The delay between registers has a **minimum** and **maximum** delay, dependent on the delays of the circuit elements


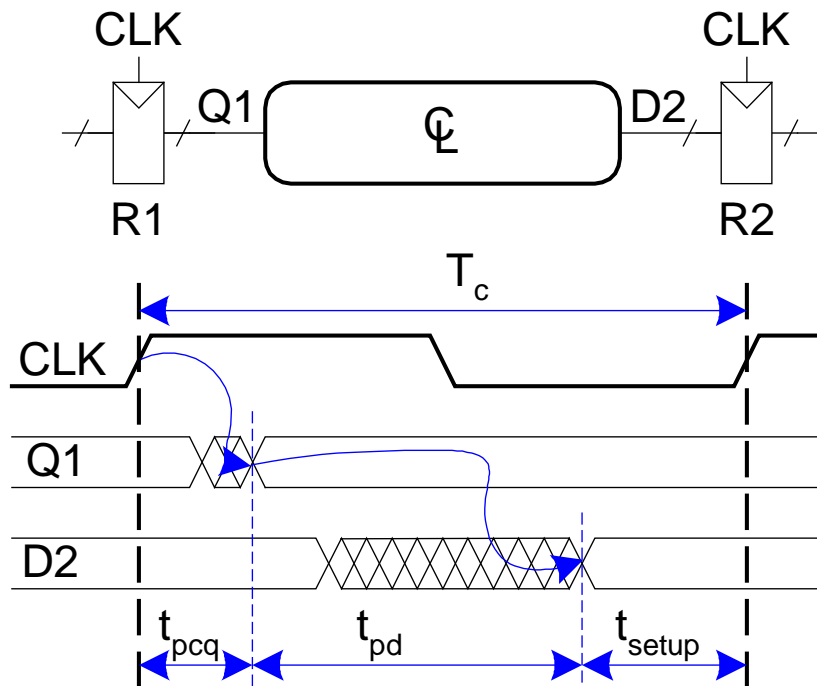
# Setup Time Constraint

- Depends on the **maximum** delay from register R1 through combinational logic to R2
- The input to register R2 must be stable at least  $t_{\text{setup}}$  before clock edge



Also called:  
**Cycle Time Constraint**


$$T_c \geq t_{pcq} + t_{pd} + t_{\text{setup}}$$
$$t_{pd} \leq T_c - (t_{pcq} + t_{\text{setup}})$$

$(t_{pcq} + t_{\text{setup}})$ :  
*sequencing overhead*


 
# Hold Time Constraint

- Depends on the **minimum** delay from register R1 through the combinational logic to R2
- The input to register R2 must be stable for at least  $t_{\text{hold}}$  after the clock edge




$$t_{\text{hold}} < t_{ccq} + t_{cd}$$

$$t_{cd} > t_{\text{hold}} - t_{ccq}$$

# Timing Analysis

- Calculate **both constraints**:
  - **Setup time** constraint (a.k.a. cycle time constraint)
  - **Hold time** constraint
- If the hold time constraint isn't met, the circuit **won't work reliably at any frequency**

# Timing Analysis Example

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 25 \text{ ps}$$

**Setup time constraint:**

$$T_c \geq t_{pcq} + t_{pd} + t_{setup}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

**Flip-Flops**

$$\left[ \begin{array}{ll} t_{ccq} & = 30 \text{ ps} \\ t_{pcq} & = 50 \text{ ps} \\ t_{setup} & = 60 \text{ ps} \\ t_{hold} & = 70 \text{ ps} \end{array} \right.$$

**Logic delays:**

**per gate**

$$\left[ \begin{array}{ll} t_{pd} & = 35 \text{ ps} \\ t_{cd} & = 25 \text{ ps} \end{array} \right.$$

**Hold time constraint:**


$$t_{ccq} + t_{cd} > t_{hold} ?$$

$$(30 + 25) \text{ ps} > 70 \text{ ps} ? \text{ No!}$$

**Won't run reliably at any frequency**

# Timing Analysis Example

Add buffers on short paths

 

$$t_{pd} = 3 \times 35 \text{ ps} = 105 \text{ ps}$$

$$t_{cd} = 2 \times 25 \text{ ps} = 50 \text{ ps}$$

Setup time constraint:

$$T_c \geq (50 + 105 + 60) \text{ ps} = 215 \text{ ps}$$

$$f_c = 1/T_c = 4.65 \text{ GHz}$$

## Timing Characteristics

Flip-Flops

$$\begin{aligned} t_{ccq} &= 30 \text{ ps} \\ t_{pcq} &= 50 \text{ ps} \\ t_{\text{setup}} &= 60 \text{ ps} \\ t_{\text{hold}} &= 70 \text{ ps} \end{aligned}$$

Logic delays:  
per gate

$$\begin{aligned} t_{pd} &= 35 \text{ ps} \\ t_{cd} &= 25 \text{ ps} \end{aligned}$$

Hold time constraint:

$$t_{ccq} + t_{cd} > t_{\text{hold}} ?$$



$$(30 + 50) \text{ ps} > 70 \text{ ps} ? \text{ Yes!}$$

# Chapter 3: Sequential Logic

## **Metastability**

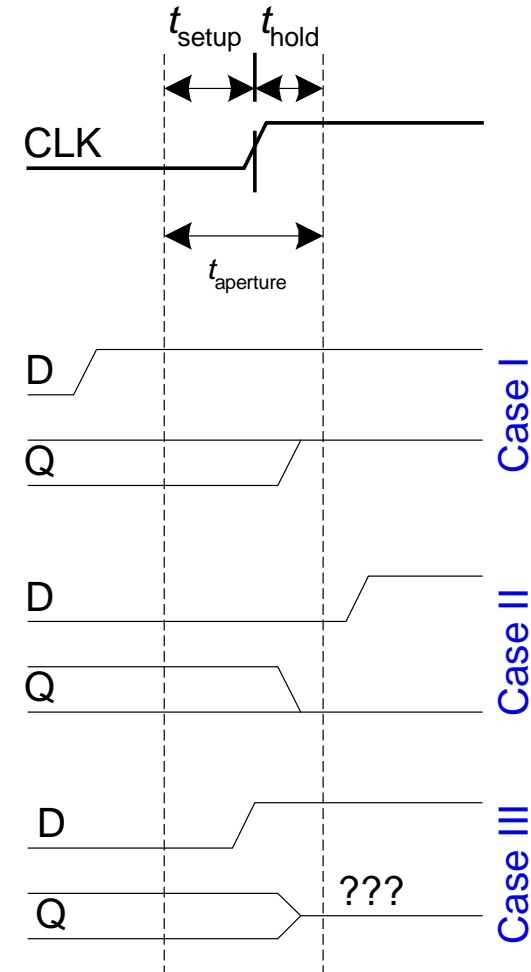 
# Violating the Dynamic Discipline

**Asynchronous** (for example, user) **inputs** might violate the dynamic discipline


 
# Metastability

- **Bistable devices:** two stable states, and a metastable state between them
- **Flip-flop:** two stable states (1 and 0) and one metastable state
- If flip-flop lands in metastable state, could stay there for an undetermined amount of time



# Chapter 3: Sequential Logic

## **Parallelism**



# Parallelism

- **Two types of parallelism:**
  - **Spatial parallelism**
    - duplicate hardware performs multiple tasks at once
  - **Temporal parallelism**
    - task is broken into multiple stages
    - also called pipelining
    - for example, an assembly line

# Parallelism

- **Token:** Group of inputs processed to produce group of outputs
- **Latency:** Time for one token to pass from start to end
- **Throughput:** Number of tokens produced per unit time

**Parallelism increases throughput**

# Parallelism Example

- Ben Bitdiddle bakes cookies to celebrate traffic light controller installation
  - **5 minutes** to roll cookies
  - **15 minutes** to bake
- What is the **latency** and **throughput** without parallelism?


**Latency** = 5 + 15 = 20 minutes = **1/3 hour**

**Throughput** = 1 tray/ 1/3 hour = **3 trays/hour**

# Parallelism Example

- What is the latency and throughput if Ben uses parallelism?
  - **Spatial parallelism:** Ben asks Allysa P. Hacker to help, using her own oven
  - **Temporal parallelism:**
    - **two stages:** rolling and baking
    - He uses two trays
    - While first batch is baking, he rolls the second batch, etc.


# Spatial Parallelism

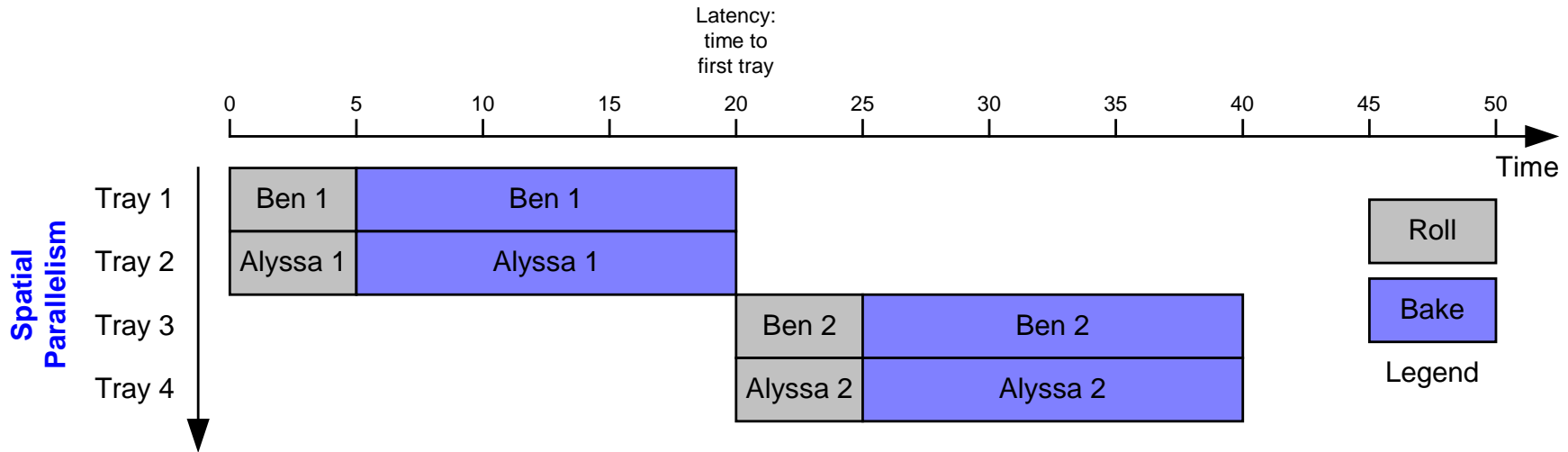

**Latency** = 5 + 15 = 20 minutes = **1/3 hour**

**Throughput** = 2 trays/ 1/3 hour = **6 trays/hour**

# Temporal Parallelism

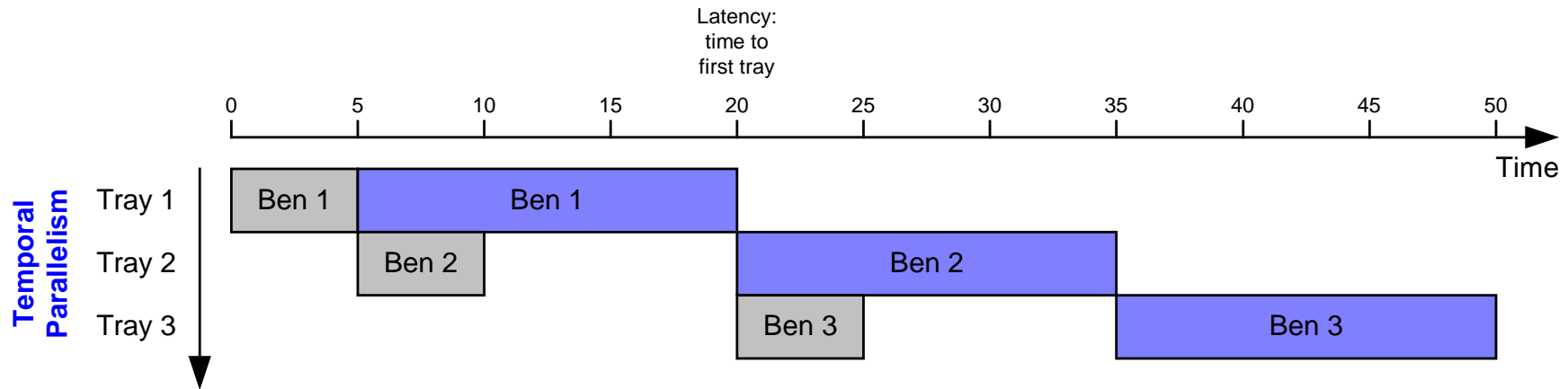

**Latency** = 5 + 15 = 20 minutes = **1/3 hour**

**Throughput** = 1 trays/ 1/4 hour = **4 trays/hour**

Using both techniques, the throughput would be **8 trays/hour**

# About these Notes

**Digital Design and Computer Architecture Lecture Notes**

**© 2021 Sarah Harris and David Harris**

**These notes may be used and modified for educational and/or non-commercial purposes so long as the source is attributed.**